

Department of Computer and Information Science
National Chiao Tung University

Digital Systems

Midterm Exam

04/21/2003

1. (10%) Simplify the following expression in sum-of-products form. Implement the simplified circuit using NAND gates.

$$\overline{A}B + \overline{B}C + \overline{A} \overline{B} \overline{C}$$

2. (8%) Find all prime implicants and essential prime implicants of

$$F(W,X,Y,Z) = \sum m(0,1,4,9,11,12,13,15)$$

3. (8%) Use two transmission gates and some inverters to implement

X	Y	F
0	0	open
0	1	1
1	0	1
1	1	0

4. (14%) Simplify the following Boolean function F together with the don't care condition d in (i) sum-of-products form, (ii) product-of-sums form:

$$F(W,X,Y,Z) = \sum m(0,1,6,15),$$

$$d(W,X,Y,Z) = \sum m(2,5,7,9,13,14)$$

5. (8%) Consider the addition of two binary numbers 0101 and 0110. Based on the concept of *carry lookahead*, find the value of P_{0-3} and G_{0-3} .
6. (16%) Consider the logic diagram shown below.
- (a) Obtain the truth table for output F . (Hint: Consider F for $A = 0$ and $A = 1$ separately.)
- (b) Give a change in inputs which will result in the longest delay for output F to change.

7. (8%) Design a combinational circuit that compares two 2-bit unsigned numbers A and B to see whether B is greater than A , using an 8-to-1 line multiplexer.
8. (10%) Perform the arithmetic operations $(+13) + (-7)$ and $(-13) - (+7)$ in binary using 5-bit signed-2's complement representation for negative numbers. Determine if there is an overflow for each of the operations.
9. (8%) What is the main difference between
 - (a) a D latch and a D flip-flop,
 - (b) a master-slave JK flip-flop and an edge-triggered JK flip-flop.
10. (10%) Obtain the characteristic table of the following edge-triggered JK flip-flop.