

Homework #4

3.13 Simplify the following expressions to (1) sum-of-products and (2) products-of-sums:

(a)* $xz' + y'z' + yz' + xy'$

3.15 Simplify the following Boolean function F , together with the don't-care conditions d , and then express the simplified function in sum-of-minterms form:

(a) $F(x, y, z) = \Sigma(0, 1, 3, 5, 7)$

$d(x, y, z) = \Sigma(2, 4, 6)$

(b)* $F(A, B, C, D) = \Sigma(0, 4, 8, 10, 14)$

$d(A, B, C, D) = \Sigma(2, 6, 12)$

3.20 Draw the multiple-level NOR circuit for the following expression:

$$F = BC(D + C)A + (BC' + DE') + BD'$$

3.24 Implement the following Boolean function F , using the two-level forms of logic

(c) NOR-OR (g) NAND-AND:

$$F(A, B, C, D) = \Sigma(1, 5, 8, 9, 10, 11, 12, 13, 15)$$

3.26 With the use of maps, find the simplest sum-of-products form of the function $F = fg$, where

$$f = abc' + b'd' + a'd' + b'cd'$$

and

$$g = (a + b + c' + d')(a' + b' + d)(a' + d')$$