6.16 Q8 Q4 Q2 Q1: 1010 1100 1110 Self correcti

Next state: 1011 1101 1111 Next state: 0100 0100 0000

$$1010 \rightarrow 1011 \rightarrow 0100$$

 $1100 \rightarrow 1101 \rightarrow 0100$
 $1110 \rightarrow 1111 \rightarrow 0000$

6.19

(a)

Present state	Next state	Flip-flop inputs				
$A_{8}A_{4}A_{2}A_{1}$	$A_{8}A_{4}A_{2}A_{1}$	$J_{A8} K_{A8}$	$J_{A4} K_{A4}$	$J_{A2} K_{A2}$	$J_{A1} K_{A1}$	
0 0 0 0	0001	0 x	0 x	0 x	1 x	
0001	0010	0 x	0 x	1 x	x 1	
0 0 1 0	0011	0 x	0 x	x 0	1 x	
0 0 1 1	0100	0 x	1 x	x 1	x 1	
0 1 0 0	0101	0 x	x 0	0 x	1 x	
0 1 0 1	0110	0 x	x 0	1 x	x 1	
0 1 1 0	0111	0 x	x 0	x 0	1 x	
0 1 1 1	1000	1 x	x 1	x 1	x 1	
1000	1001	x 0	0 x	0 x	1 x	
1001	0000	x 1	0 x	0 x	x 1	

$$\begin{split} J_{A1} &= I \\ K_{A1} &= I \\ J_{A2} &= A_1 A'_8 \\ K_{A2} &= A_1 \\ J_{A4} &= A_1 A_2 \\ K_{A4} &= A_1 A_2 \\ J_{A8} &= A_1 A_2 A_4 \\ K_{A8} &= A_1 \end{aligned}$$

$$d(A_8, A_4, A_2, A_1) = \Sigma (10, 11, 12, 13, 14, 15)$$

6.19 (b) From the state table in Table 6.5:

$$D_{O1} = Q'_1$$

$$D_{Q2} = \sum (1, 2, 5, 6)$$

$$D_{Q4} = \sum (3, 4, 5, 6)$$

$$D_{Q8} = \sum (7,8)$$

Don't care: $d = \sum (10, 11, 12, 13, 14, 15)$

Simplifying with maps:

$$D_{Q2} = Q_2 Q_1' + Q_8 Q_2' Q_1$$

$$D_{Q4} = Q_4 Q'_1 + Q_4 Q'_2 + Q'_4 Q_2 Q_1$$


$$D_{Q8} = Q_8 Q'_1 + Q_4 Q_2 Q_1$$

Using JK flip-flops is the most efficient.

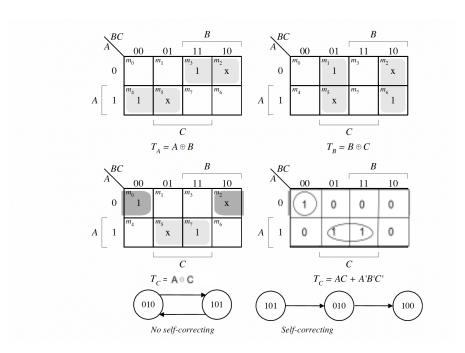6.21 (a)
$$J_{A0} = LI_0 + L'C KA_0 = LI'_0 + L'C$$
 (b)
$$J = [L(LI)']'(L+C) = (L'+LI)(L+C)$$

$$LI + L'C + LIC = LI + L'C (use a map)$$

$$K = (LI)'(L+C) = (L'+I')(L+C) = LI' + L'C$$



Present state			Next state			FF inputs		
Α	В	С	Α	В	С	TA	ТВ	TC
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0

0	1	0	1	0	0	1	1	0
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	1	0	1	0	1	1	1
1	1	0	1	0	0	0	1	0
1	1	1	1	1	0	0	0	1

