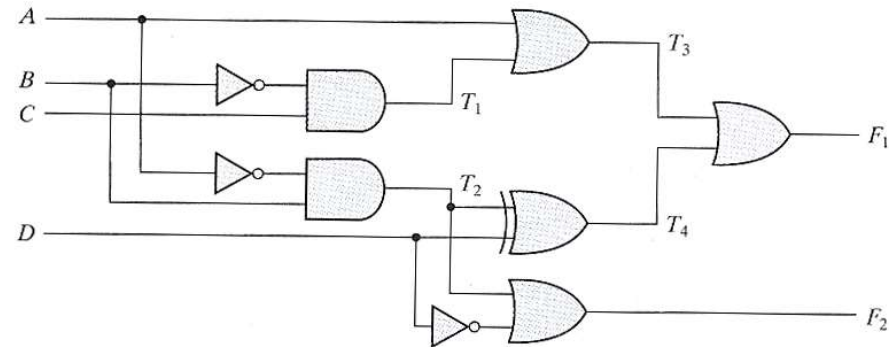


# Homework #5

**4.1** Consider the combinational circuit



Derive the Boolean expressions for  $T_1$  through  $T_4$ . Evaluate the outputs  $F_1$  and  $F_2$  as a function of the four inputs.

**4.4** Design a combinational circuit with three inputs and one output.

(a)\* The output is 1 when the binary value of the inputs is less than 3 and greater than 6. The output is 0 otherwise.

**4.8** Design a code converter that converts a decimal digit from

(a)\* The 8, 4, -2, -1 code to BCD.

**4.14\*** Assume that the exclusive-OR gate has a propagation delay of 10 ns and that the AND or OR gates have a propagation delay of 5 ns. What is the total propagation delay time in the four-bit adder of Fig. 4.12?

**4.18** Design a combinational circuit that generates the 9's complement of a

(a)\* BCD digit.