

Homework #7

5.1 ✓

The D latch of Fig. 5.6 is constructed with four NAND gates and an inverter. Consider the following three other ways for obtaining a D latch. In each case, draw the logic diagram and verify the characteristic table for each.

(b) Use only NOR gates.

5-11

5.2 ✓

Construct a JK flip-flop using a D flip-flop, a two-to-one-line multiplexer, and an inverter.

5-23

5.6

A sequential circuit with two D flip-flops A and B , two inputs, x and y ; and one output z is specified by the following next-state and output equations (HDL—see Problem 5.35):

$$A(t + 1) = xy' + xB$$

$$B(t + 1) = xA + xB'$$

$$z = A$$

- (a) Draw the logic diagram of the circuit.
- (b) List the state table for the sequential circuit.
- (c) Draw the corresponding state diagram.

- 5.8* Derive the state table and the state diagram of the sequential circuit shown in Fig. P5.8. Explain the function that the circuit performs.

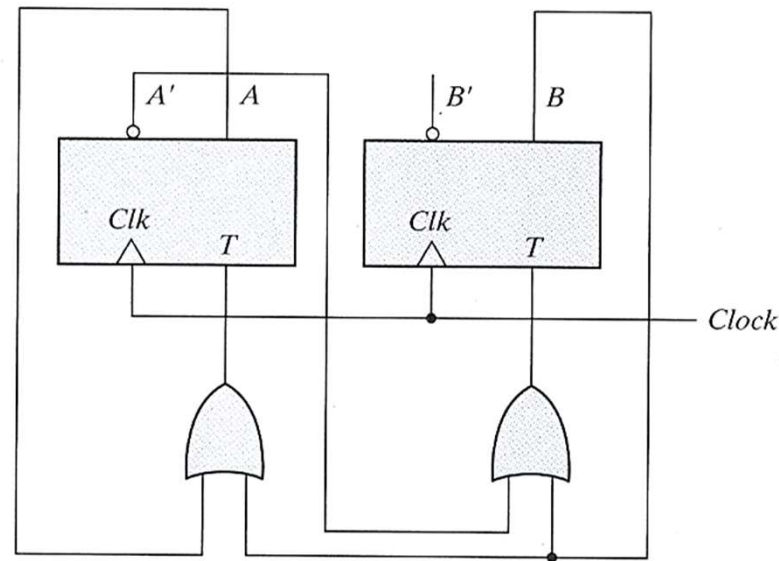


FIGURE P5.8

- 5.10 A sequential circuit has two *JK* flip-flops *A* and *B*, two inputs *x* and *y*, and one output *z*. The flip-flop input equations and circuit output equation are

$$J_A = Bx + B'y' \quad K_A = B'x + y$$





$$J_B = A'x \quad K_B = A + xy'$$

$$z = (A + B)x'y'$$

- Draw the logic diagram of the circuit.
- Tabulate the state table.

5-1


111652017 廖修远

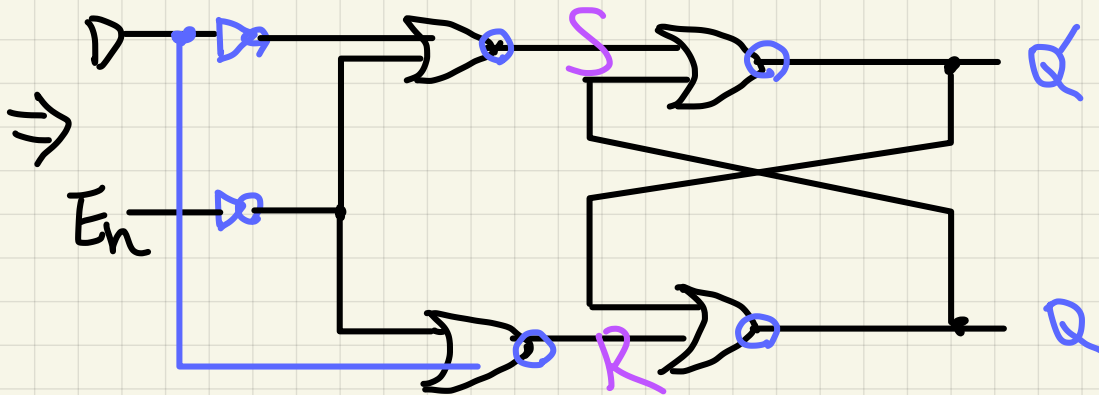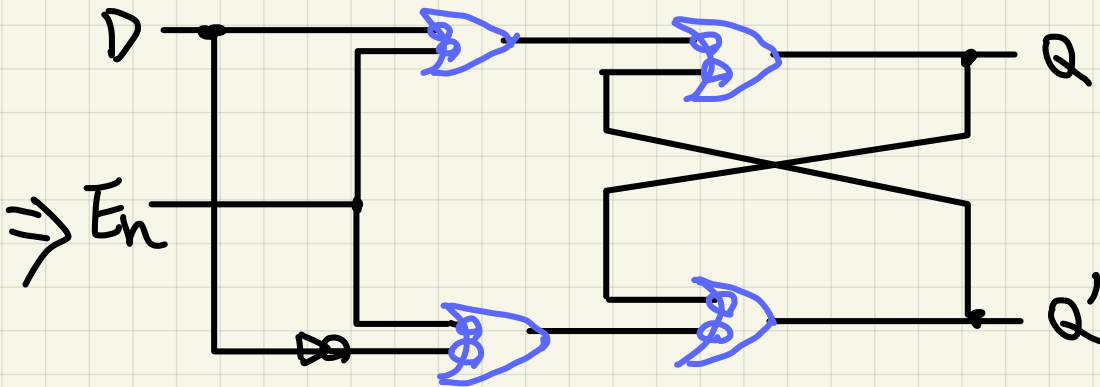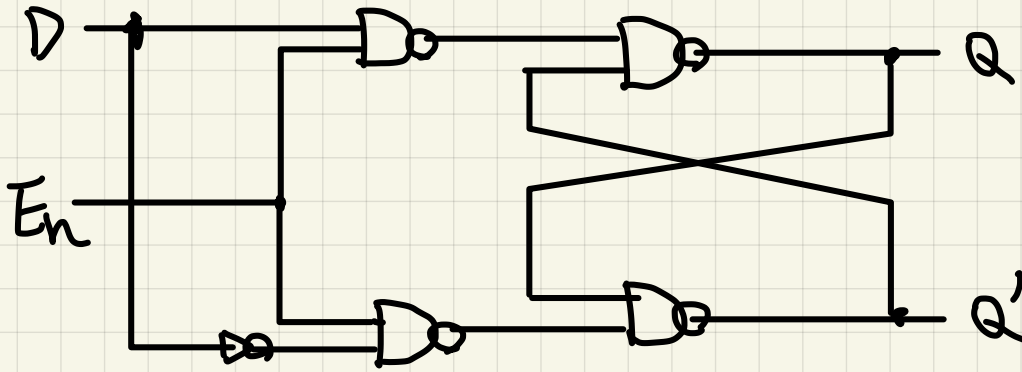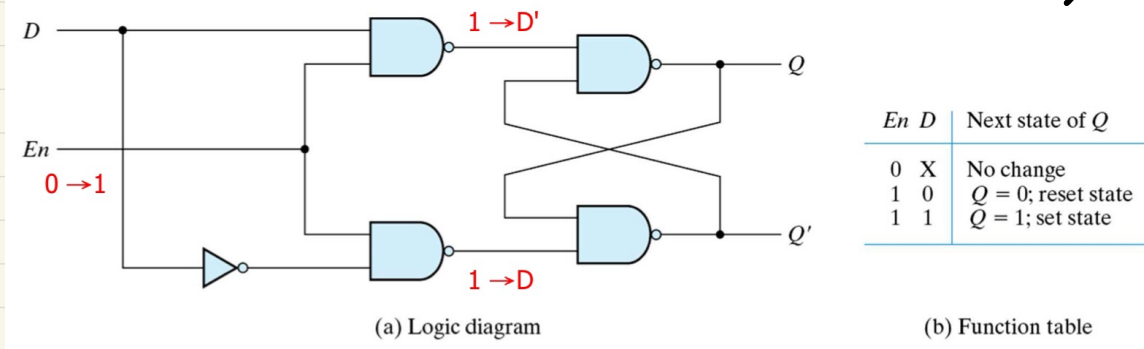


State table

En	D	S	R	next Q
0	X	0	0	no change
1	0	0	1	Q = 0 (reset)
1	1	1	0	Q = 1 (set)

5.2

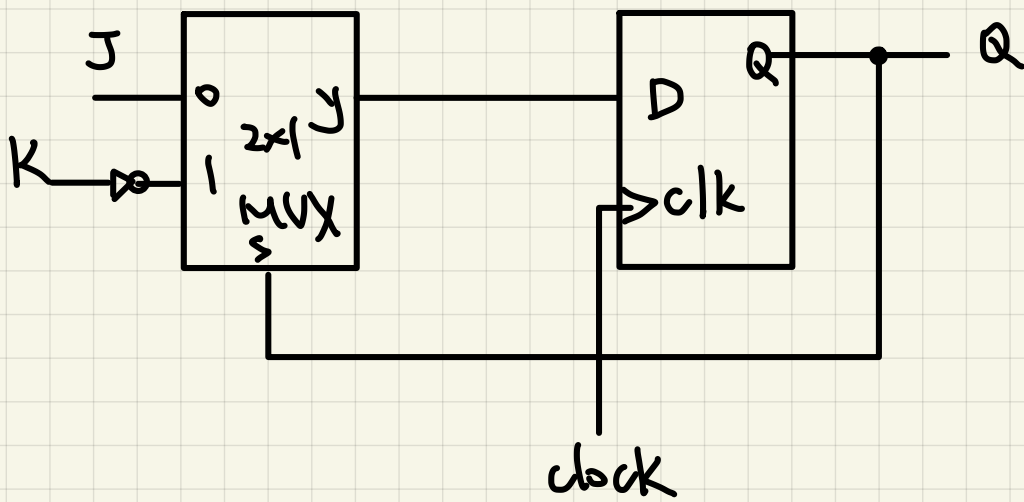

5.6 (a)

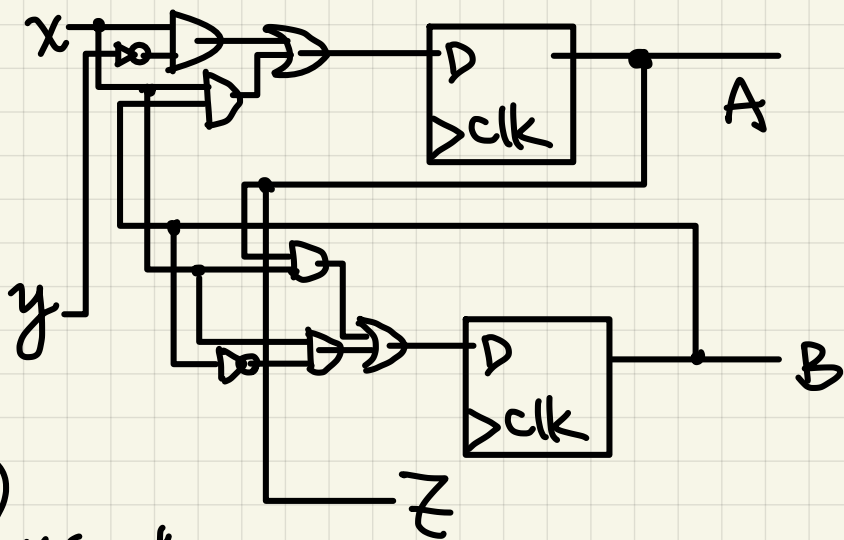

(b)

present

next

A

B

x

予

A

B

乙

0000000000

0000-0000


--DO--DO--DO--DO

0-0-0-0-0-0-0-0

00-00-00-00

00-0000-00

000000

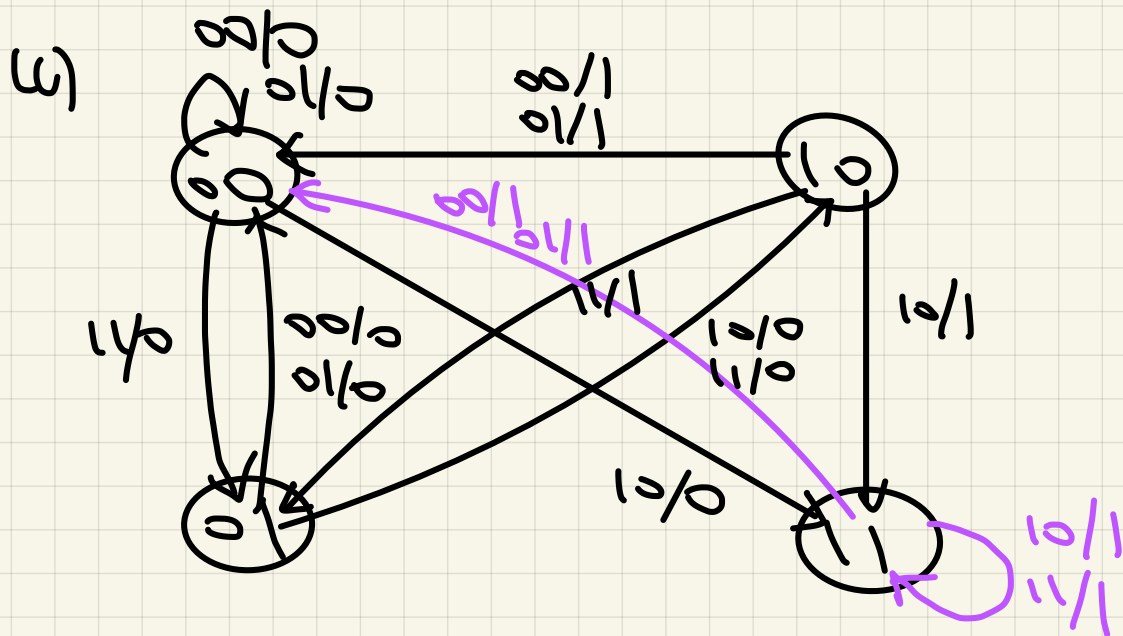

5.8 $T_A = \cancel{AB} A + B$
 $T_B = \cancel{A'B} A' + B$

$A(t+1) = A(t) \oplus T_A$

$B(t+1) = B(t) \oplus T_B$

present


A	B	T_A	T_B
0	0	0	0
0	1	0	1
1	0	1	0
1	1	1	1

next


A	B
0	0
0	1
1	0
1	1

Annotations: Blue arrows indicate 'no change' from 00 to 01 and 10 to 11. Pink arrows indicate 'reset' from 01 to 00 and 11 to 10. Pink arrows indicate 'set' from 10 to 11 and 11 to 00.

→ 01 → 10 → 00

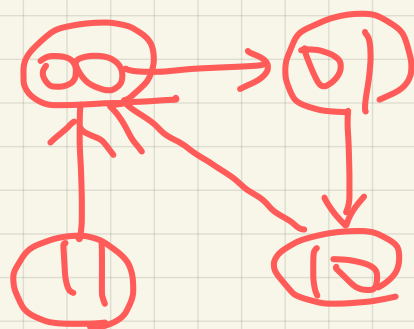

5.10 (a)

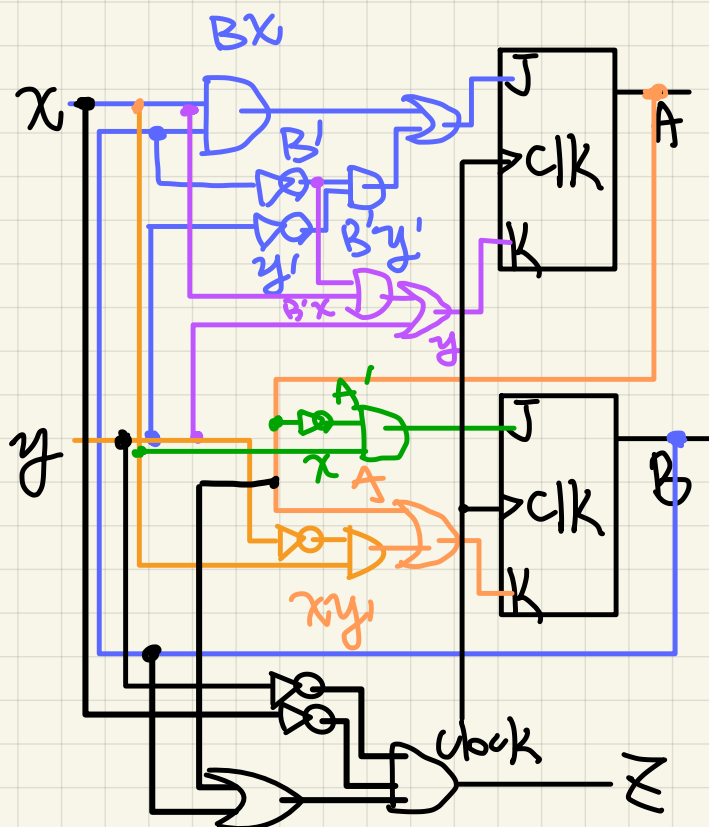

5.10(b)

[illegible]