



Department of Computer Science
National Chiao Tung University
Digital System Design

Second Midterm Exam

12/06/2012

✓ 1. (10%) Derive the optimal (simplified) two-level NOR-OR implementation of $f(x,y,z) = x'y'z' + x'z + y'z$.

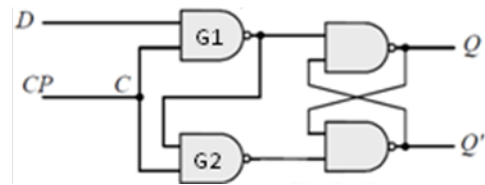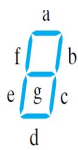✓ 2. (18%) Consider the following display (left) for BCD-to-seven-segment decoder.
(a) Implement **a**, **b**, **c**, **d** using a decoder and external gates (with least wires).
(b) Implement **e** with an 8x1 multiplexer and an inverter.



✗ 3. (10%) Consider the above circuit (right). Obtain the output values of G1 and G2 for different values of CP and D inputs to show that it is a D-latch.

✓ 4. (10%) Implement a four-bit (even) parity generator using a 4x1 multiplexer and minimum number of logic gates.

✓ 5. (10%) Design a code converter that converts a decimal digit from the 2421 code to BCD, with $d(w,x,y,z) = \sum(5,6,7,8,9,10)$.

✗ 6. (16%) Consider a sequential circuit with a D flip-flop A, a JK flip-flop B, an input x, and an output z, with the following input/output equations

$$D_A = Ax', \quad J_B = x, \quad K_B = Ax + B, \quad z = Bx'$$


Derive the state table of the circuit.

✗ 7. (18%) Derive the state table and state diagram of a sequential circuit with three T flip-flops (A, B, and C), as described by the three input equations:

$$T_A = BC, \quad T_B = C, \quad T_C = 1.$$

Assume that each flip-flop has a propagation delay of 15ns, a setup time of 10ns, a hold time of 5ns, and the AND gate has a propagation delay of 5ns. Obtain the maximum clock frequency that the circuit can operate correctly (according to the state diagram).

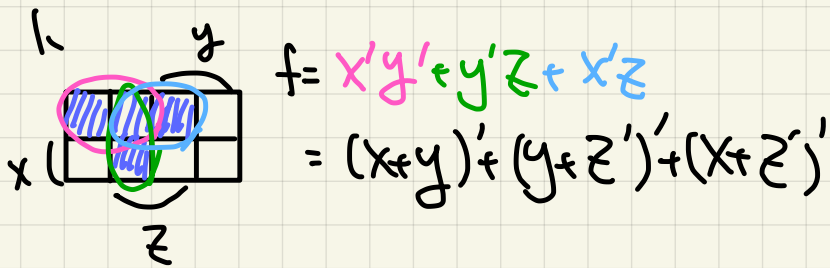✗ 8. (8%) Explain the purpose of the *carry lookahead* logic for a binary adder. Give the carry output of the second stage of a 4-bit adder as a function of input carry C_0 and carry generate/propagate signals.



4.4 B C D F

0 0 0 0 0

0 0 0 1 1 $F = (C \oplus D)$

0 0 1 0 1

0 0 1 1 0

0 1 0 0 1

0 1 0 1 0 $F = (C \oplus D)'$

0 1 1 0 0

0 1 1 1 1

1 0 0 0 1

1 0 0 1 0 $F = (C \oplus D)'$

1 0 1 0 0


1 0 1 1 1

1 1 0 0 0

1 1 0 1 1 $F = (C \oplus D)$

1 1 1 0 1

1 1 1 1 0

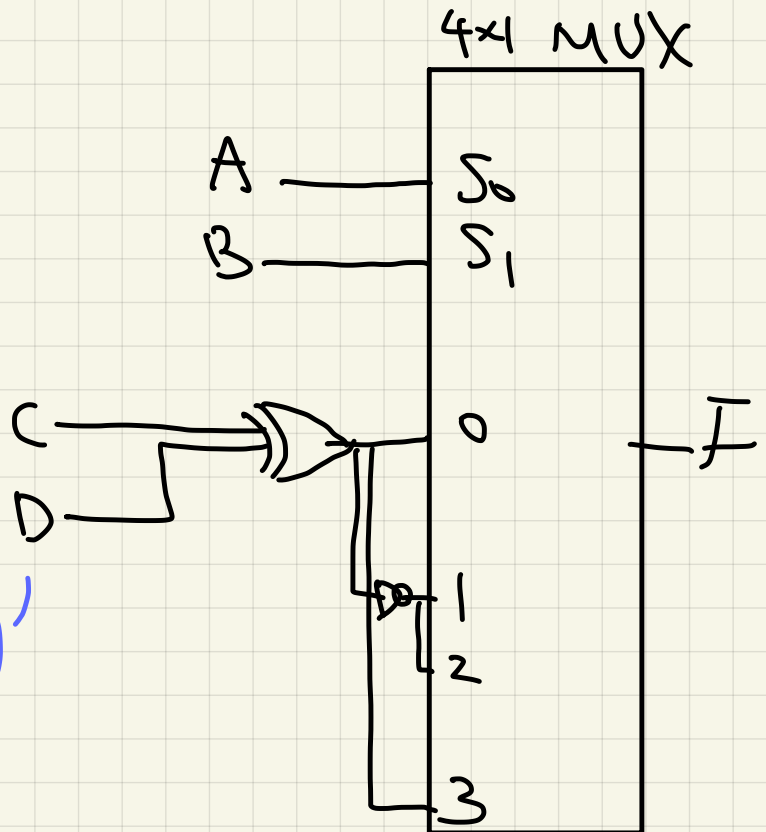

5.