

# Homework #4

**3.13** Simplify the following expressions to (1) sum-of-products and (2) products-of-sums:

(a)\*  $xz' + y'z' + yz' + xy'$

**3.15** Simplify the following Boolean function  $F$ , together with the don't-care conditions  $d$ , and then express the simplified function in sum-of-minterms form:

(a)  $F(x, y, z) = \Sigma(0, 1, 3, 5, 7)$

$d(x, y, z) = \Sigma(2, 4, 6)$

(b)\*  $F(A, B, C, D) = \Sigma(0, 4, 8, 10, 14)$

$d(A, B, C, D) = \Sigma(2, 6, 12)$

**3.20** Draw the multiple-level NOR circuit for the following expression:

$$F = BC(D + C)A + (BC' + DE') + BD'$$

**3.24** Implement the following Boolean function  $F$ , using the two-level forms of logic

(c) NOR-OR (g) NAND-AND:

$$F(A, B, C, D) = \Sigma(1, 5, 8, 9, 10, 11, 12, 13, 15)$$

**3.26** With the use of maps, find the simplest sum-of-products form of the function  $F = fg$ , where


$$f = abc' + b'd' + a'd' + b'cd'$$

and

$$g = (a + b + c' + d')(a' + b' + d)(a' + d')$$

$g' = a'b'cd + abd' + ad$  (不要有重复)

3.13 (1) SOP

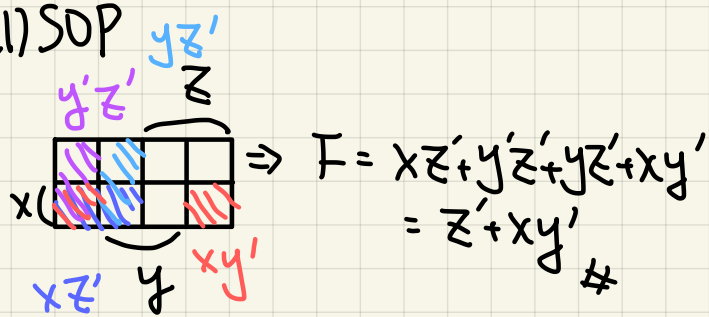


(2) POS


$$F' = (xz' + yz' + yz + xy')' = yz + x'z$$

$$\Rightarrow F = (y' + z')(x + z')$$

3.15 (a) y

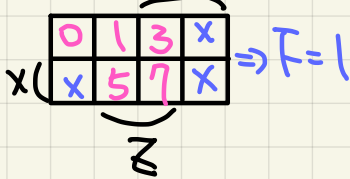


3.15(b)

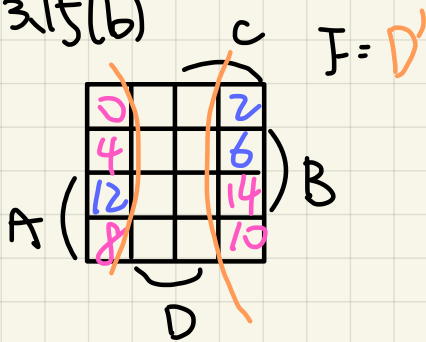


3.20

$$F = \cancel{ABCD} + ABC + BC'D + DE' + BD'$$

$$(A' + B' + C')'$$

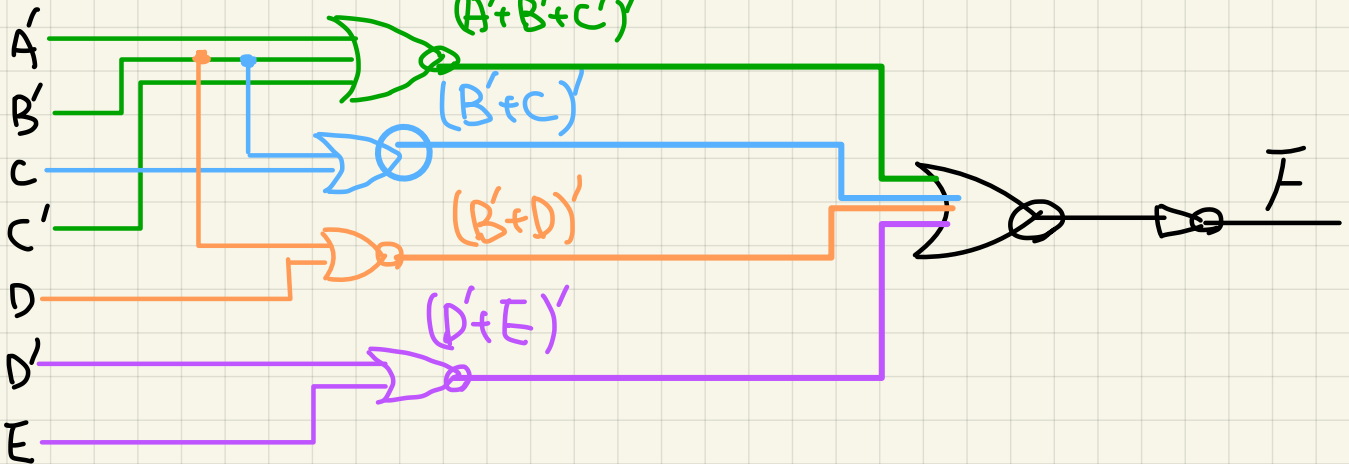


3,24(L)

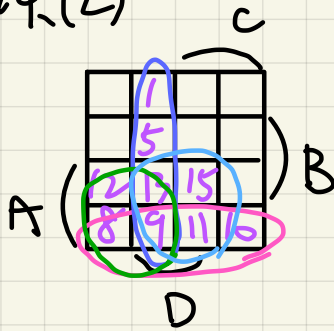


$$F = AB' + C'D + AC' + AD$$

$$= (A+B)' + (C+D)' + (A+C)' + (A+D)'$$

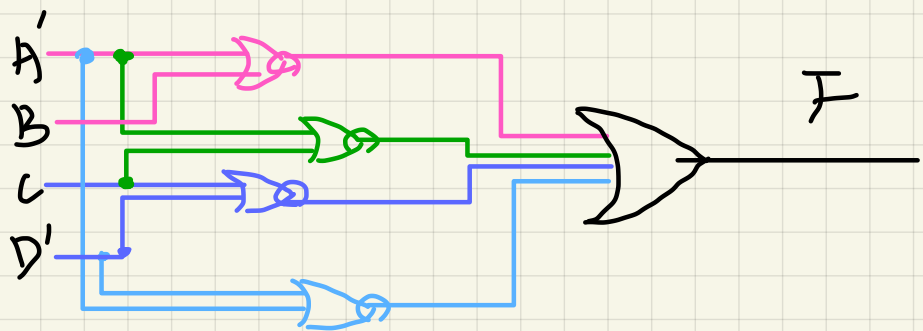


3,24(g)



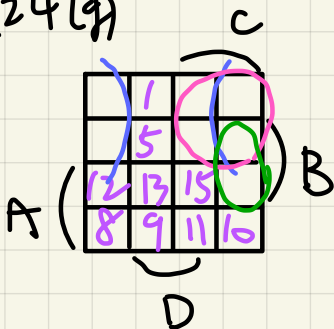


$$F' = A'D' + A'C + BCD'$$

$$\Rightarrow F = (A'D')'(A'C)'(BCD')'$$

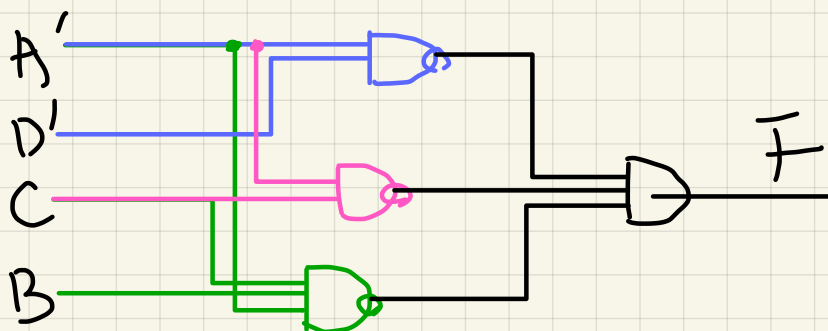

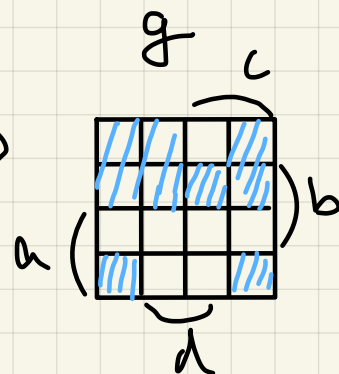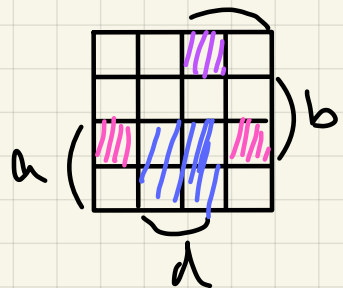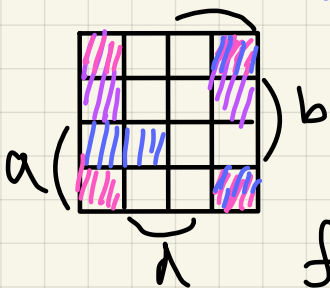326 f  $abc' + b'd' + a'd'$   $g' = a'b'cd + abd' + ad$



$$F = b'd' + a'd'$$

