

# Homework #6


✓

A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise.

(a)\* Design a 3-input majority circuit by finding the circuit's truth table, Boolean equation, and a logic diagram.

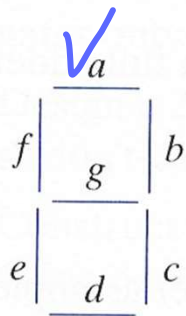4.9

An ABCD-to-seven-segment decoder is a combinational circuit that converts a decimal digit in BCD to an appropriate code for the selection of segments in an indicator used to display the decimal digit in a familiar form. The seven outputs of the decoder ( $a, b, c, d, e, f, g$ ) select the corresponding segments in the display, as shown in Fig. P4.9(a). The numeric display chosen to represent the decimal digit is shown in Fig. P4.9(b). Using a truth table and Karnaugh maps, design the BCD-to-seven-segment decoder using a minimum number of gates. The six invalid combinations should result in a blank display. (HDL—see Problem 4.51.)



(a) Segment designation



(b) Numerical designation for display

**FIGURE P4.9**

✓✓ 4.12 Design a half-subtractor circuit with inputs  $x$  and  $y$  and outputs  $Diff$  and  $B_{out}$ . The circuit subtracts the bits  $y - x$  and places the difference in  $D$  and the borrow in  $B_{out}$ .

✓ (a) Design a full-subtractor circuit with three inputs  $x, y, B_{in}$  and two outputs  $Diff$  and  $B_{out}$ . The circuit subtracts  $y - x - B_{in}$ , where  $B_{in}$  is the input borrow,  $B_{out}$  is the output borrow, and  $Diff$  is the difference.

✓ 4.18 Using a decoder constructed with NAND gates (similar to Fig. 4.19) and external gates, design the combinational circuit defined by the following three Boolean functions:

✓ (a)  $F_1 = xy + xz' + yz'$

$$F_2 = xz + xy + yz$$

$$F_3 = y'z + x'y'z' + xy$$

67, 46, 26 =  $\Sigma(2, 4, 6, 7) = F_1$

✓ 4.35 Implement the following Boolean function with a  $4 \times 1$  multiplexer and external gates.

Q ✓ (a)\*  $F_1(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$

P.53

8x1 ?  
2x1 ?

4.6 x y z Output

0 0 0 0

0 0 1 0

0 1 0 0


1 0 0 0

6 1 1 0


5 1 0 1

3 0 1 1


7 1 1 1

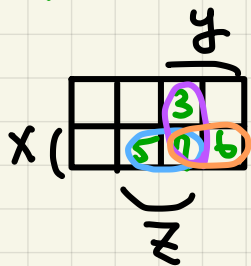

$$F = xz + yz + xy$$

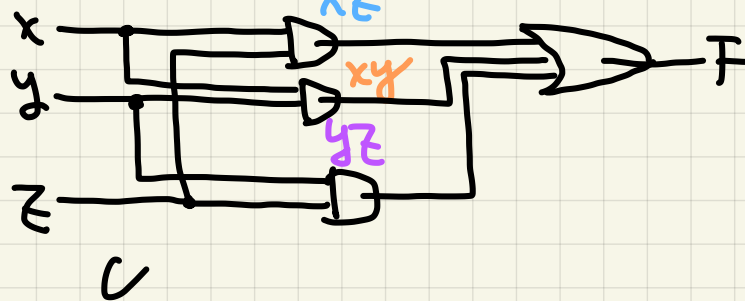

4.9 (a)

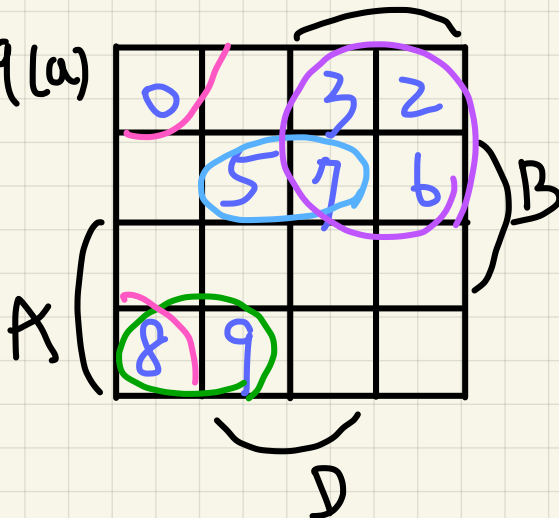

$$a = AB'C' + A'BD + B'C'D' + A'C$$

## 4.12 ① half-subtractor


x y D Bout

0 0 0 0

0 1 1 0

1 0 1 1

1 1 0 0

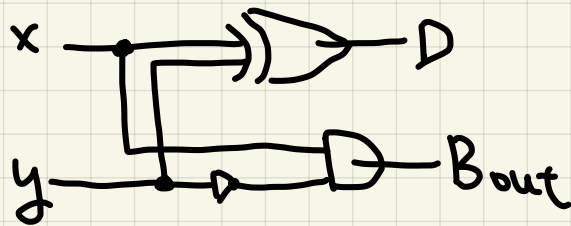

$$\Rightarrow D = x \oplus y = xy' + x'y$$

$$B_{out} = xy'$$

借後的 diff 借 =

② x y B<sub>in</sub> D Bout

0 0 0 0 0

0 0 1 1 1

0 1 0 1 0

0 1 1 0 0

1 0 0 1 1

1 0 1 ~~1~~ 1



1 1 0 0 0

1 1 1 1 1

428 (a)  $F_1 = (m_2 + m_4 + m_6 + m_7)$   
 $= (m'_2 m'_4 m'_6 m'_7)'$

$F_2 = (m_3 + m_5 + m_6 + m_7)$   
 $= (m'_3 m'_5 m'_6 m'_7)'$

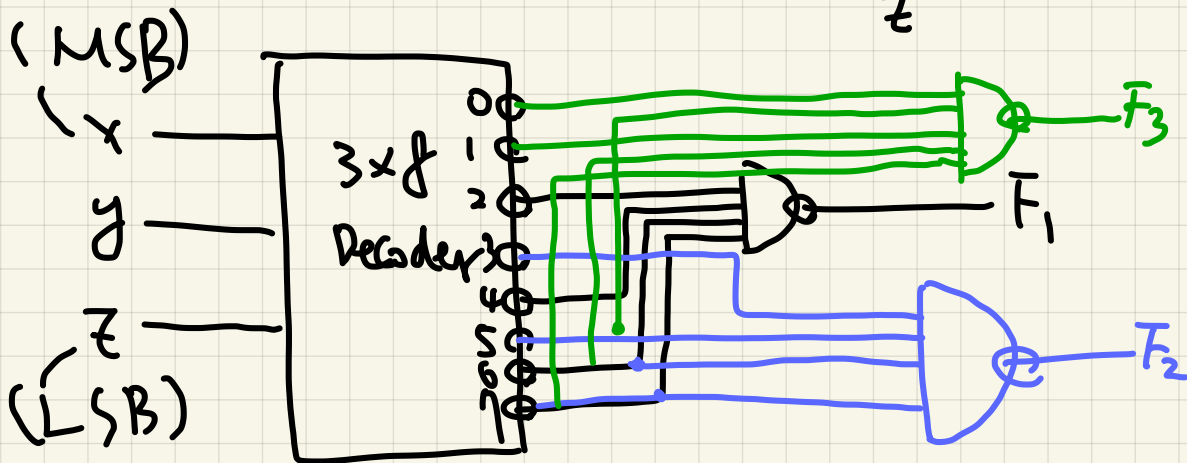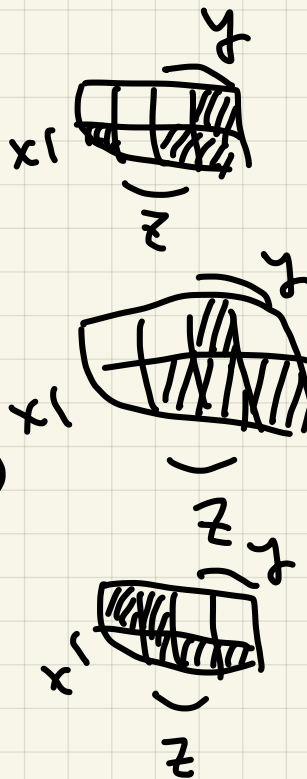$F_3 = (m_0 + m_1 + m_5 + m_6 + m_7)$   
 $= (m'_0 m'_1 m'_5 m'_6 m'_7)'$



4.35(a)

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$AB=00$

$F=D$

$AB=01$

$F=C'D'$   
 $=(C+D)'$

$AB=10$

$F=CD$

$AB=11$

$F=1$

