

Homework #10

- 6.16* The BCD ripple counter shown in Fig. 6.10 has four flip-flops and 16 states, of which only 10 are used. Analyze the circuit and determine the next state for each of the other six unused states. What will happen if a noise signal sends the circuit to one of the unused states?
- 6.19 The flip-flop input equations for a BCD counter using T flip-flops are given in Section 6.4. Obtain the input equations for a BCD counter that uses (a) JK flip-flops and (b) $*D$ flip-flops. Compare the three designs to determine which one is the most efficient.
- 6.21* The counter of Fig. 6.14 has two control inputs—*Load* (L) and *Count* (C)—and a data input, (I_i).
- (a) Derive the flip-flop input equations for J and K of the first stage in terms of L , C , and I .
- (b) The logic diagram of the first stage of an equivalent circuit is shown in Fig. P6.21. Verify that this circuit is equivalent to the one in (a).


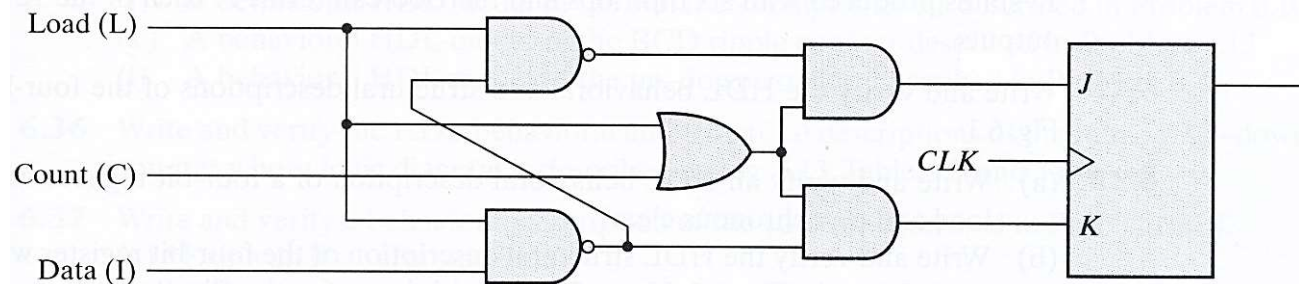


FIGURE P6.21


6.24* Design a counter with T flip-flops that goes through the following binary repeated sequence: 0, 1, 3, 7, 6, 4. Show that when binary states 010 and 101 are considered as don't care conditions, the counter may not operate properly. Find a way to correct the design.

6.28 Using D flip-flops,
(a) *Design a counter with the following repeated binary sequence: 0, 1, 2, 4, 6.


6.16

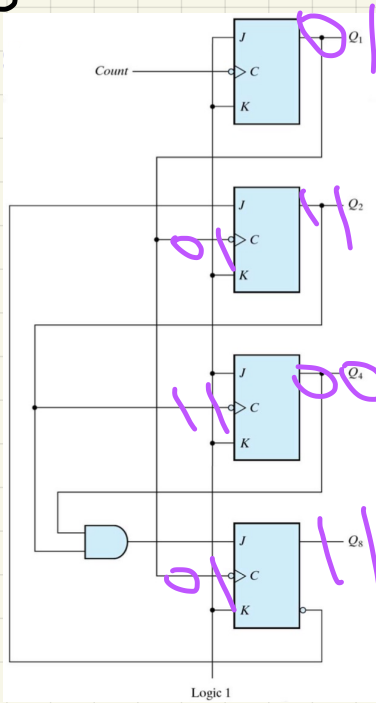


1010 → 1011

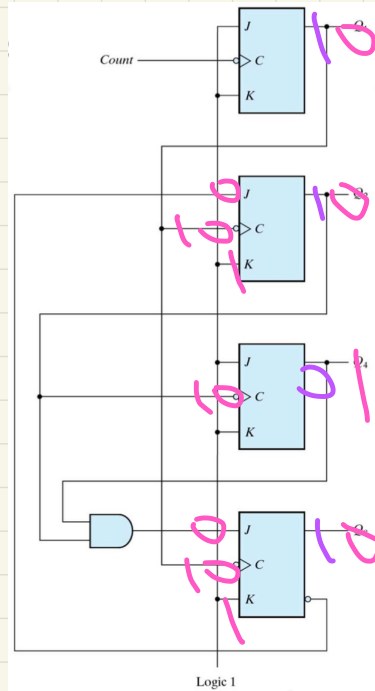


1011 → 0100

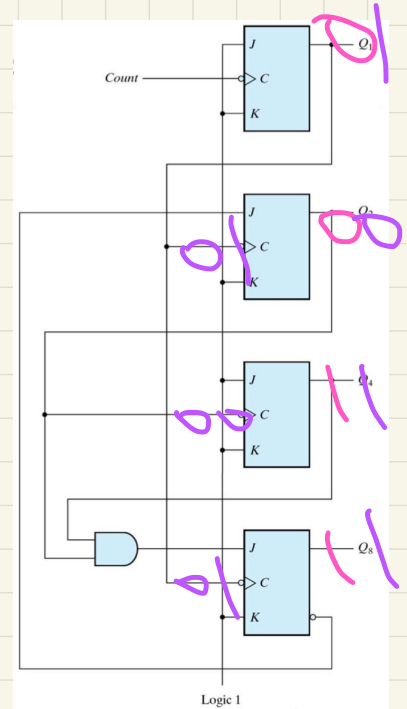


0100 → 0101

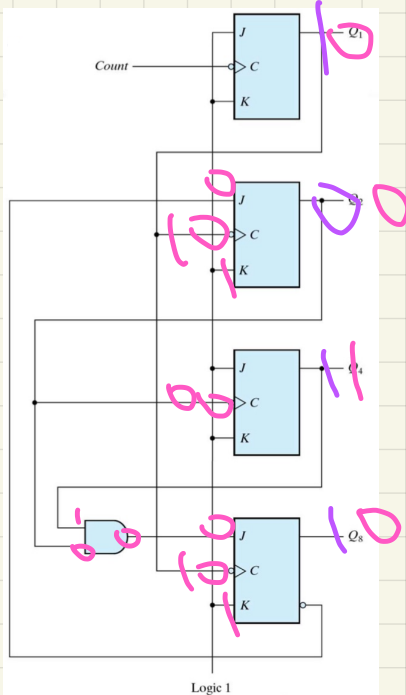

0101 → 0100

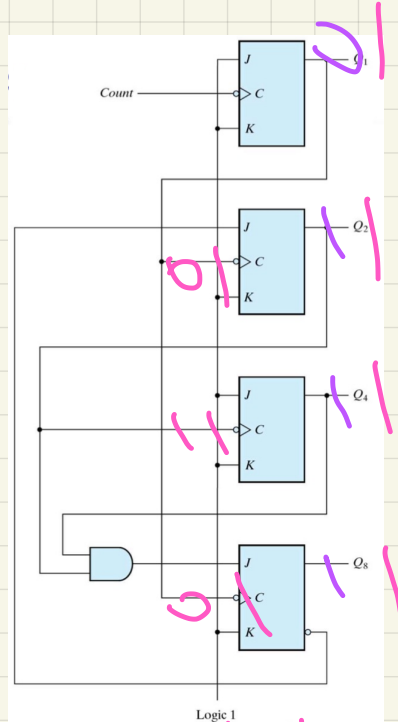

0100 → 1111

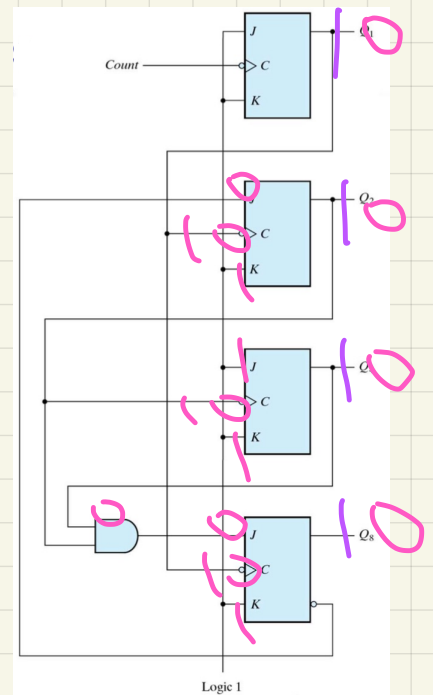

1111 → 0000

explan: 一次修正 = 1011, 1101, 1111

二次修正 = 1010, 1100, 1110

619 JJK-Flip-Flop

Ex. BCD counters

Present State				Next State				Output	Flip-Flop Inputs			
Q ₈	Q ₄	Q ₂	Q ₁	Q ₈	Q ₄	Q ₂	Q ₁	y	TQ ₈	TQ ₄	TQ ₂	TQ ₁
0	0	0	0	0	0	0	1	0				
0	0	0	1	0	0	1	0	0				
0	0	1	0	0	0	1	1	0				
0	0	1	1	0	1	0	0	0				
0	1	0	0	0	1	0	1	0				
0	1	0	1	0	1	1	0	0				
0	1	1	0	0	1	1	1	1				
0	1	1	1	1	0	0	0	0				
1	0	0	0	1	0	0	1	0				
1	0	0	1	0	0	0	0	1				

Excitation table

Q	Q(t+1)	J	K
0	0	x	x
0	1	x	0
1	0	0	x
1	1	x	x

present state

next state

Flip-Flop

Q₈ Q₄ Q₂ Q₁

Q₈ Q₄ Q₂ Q₁

J₈ K₈ J₄ K₄ J₂ K₂ J₁ K₁

0	0	0	0	0	0	0	0	0	x	0	x	x	x
1	0	0	0	0	0	0	1	0	x	0	x	x	x
2	0	0	1	0	0	0	0	0	x	x	x	x	x
3	0	0	1	1	0	0	0	0	x	x	x	x	x
4	0	1	0	0	0	1	0	0	x	x	x	x	x
5	0	1	0	1	0	1	0	0	x	x	x	x	x
6	0	1	1	0	0	1	1	1	x	x	x	x	x
7	0	1	1	1	1	0	0	0	x	x	x	x	x
8	1	0	0	0	1	0	0	1	x	x	x	x	x
9	1	0	0	1	0	0	0	0	x	x	x	x	x

J₈

x	x	1	x	x
x	x	x	x	x

Q₈ (Q₄ Q₂ Q₁)

K₈

x	x	x	x	x
x	x	x	x	x

Q₈ (Q₁)

J₄

x	x	1	x	x
x	x	x	x	x

Q₈ (Q₂ Q₁)

K₄

x	x	1	x	x
x	x	x	x	x

Q₈ (Q₂ Q₁)

J₂




1	x	x	x	x
x	x	x	x	x

Q₈ (Q₈' Q₁)

K₂

x	x	1	x	x
x	x	x	x	x

Q₈ (Q₁)

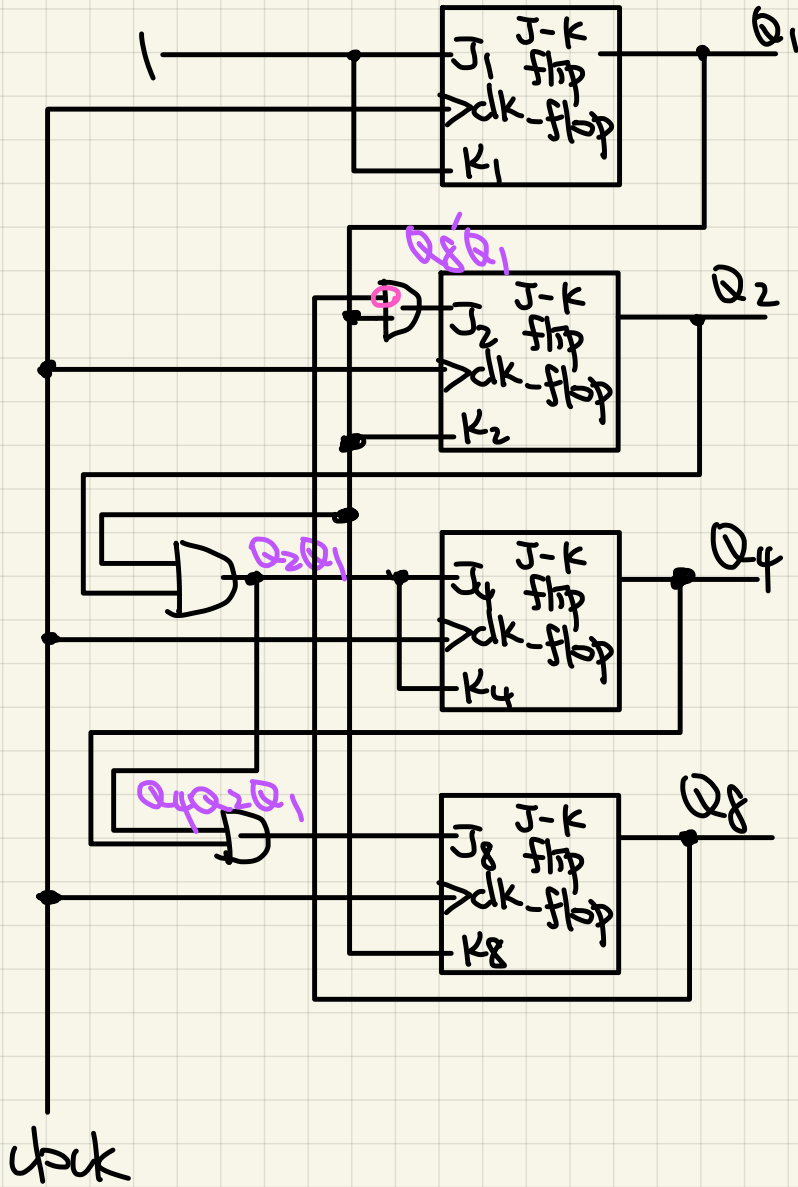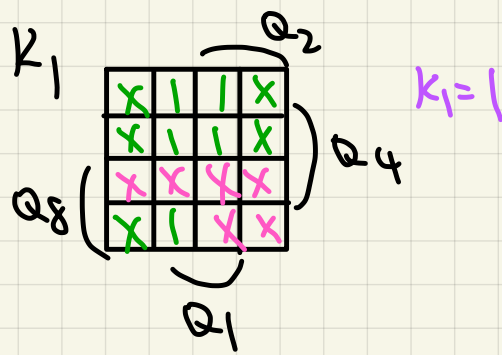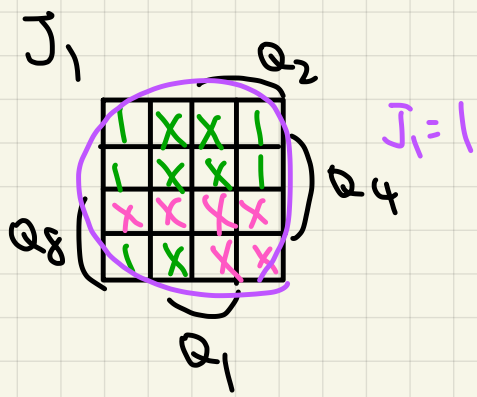

Logic equations for J and K inputs:

- $J_8 = Q_4 Q_2 Q_1 \checkmark$
- $J_4 = Q_2 Q_1 \checkmark$
- $J_2 = Q_8' Q_1 \checkmark$
- $J_1 = 1 \checkmark$
- $K_8 = Q_1 \checkmark$
- $K_4 = Q_2 Q_1 \checkmark$
- $K_2 = Q_1 \checkmark$
- $K_1 = 1 \checkmark$

619 (D-Flip-Flop)

Ex. BCD counters

Present State				Next State				Output	Flip-Flop Inputs			
Q ₈	Q ₄	Q ₂	Q ₁	Q ₈	Q ₄	Q ₂	Q ₁	Y	TQ ₈	TQ ₄	TQ ₂	TQ ₁
0	0	0	0	0	0	0	1	0				
0	0	0	1	0	0	1	0	0				
0	0	1	0	0	0	1	1	0				
0	0	1	1	0	1	0	0	0				
0	1	0	0	0	1	0	1	0				
0	1	0	1	0	1	1	0	0				
0	1	1	0	0	1	1	1	0				
0	1	1	1	1	0	0	0	0				
1	0	0	0	1	0	0	1	0				
1	0	0	1	0	0	0	0	1				

excitation table

Q
 $Q(t+1)$
 D

present state				next state				Flip-Flop			
Q ₈	Q ₄	Q ₂	Q ₁	Q ₈	Q ₄	Q ₂	Q ₁	D ₈	D ₄	D ₂	D ₁
0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	1	0	0	1	0	0	0	0	0
0	0	1	0	0	0	1	1	0	0	0	0
0	0	1	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	1	0	0	0	0
0	1	0	1	0	1	1	0	0	0	0	0
0	1	1	0	0	1	1	1	0	0	0	0
0	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	1	0	0	1	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0

D_8

 $D_8 = Q_4 Q_2 Q_1 + Q_8 Q_1'$

D_4

 $D_4 = Q_4 Q_2' + Q_4' Q_2 Q_1 + Q_4 Q_1'$

D_2

 $D_2 = Q_2 Q_1' + Q_8' Q_2 Q_1$

D_1


 $D_1 = Q_1'$

$$D_8 = Q_4 Q_2 Q_1 + Q_8 Q_1' \quad \checkmark$$

$$D_4 = Q_4 Q_2' + Q_4' Q_2 Q_1 + Q_4 Q_1' = Q_4 (Q_1' + Q_2') + Q_4' Q_2 Q_1$$


$$D_2 = Q_2 Q_1' + Q_8 Q_2' Q_1 \quad \checkmark$$

$$D_1 = Q_1' \quad \checkmark$$

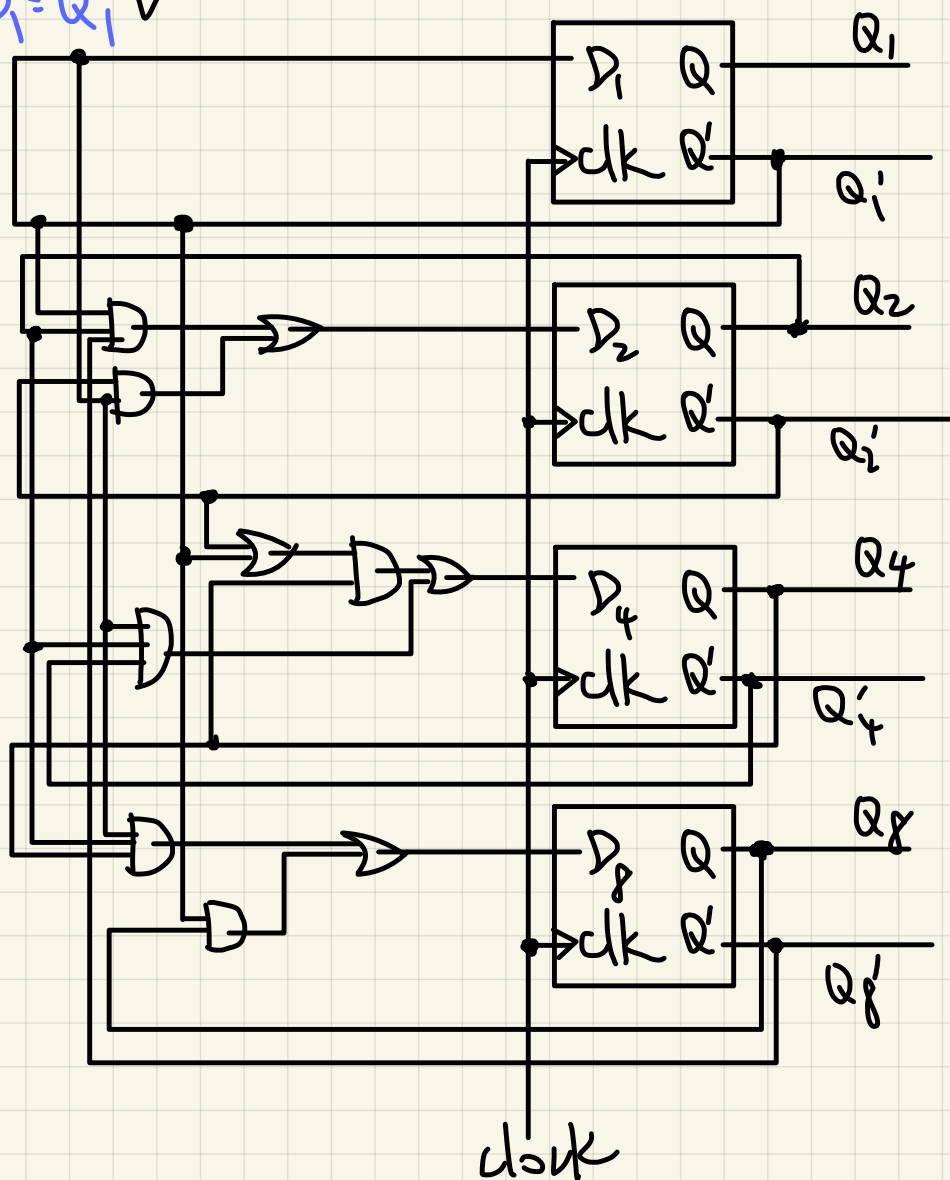



JK flip-flops 最有效率：只有三個gate
且 1 level (delay 最小) □

6.21

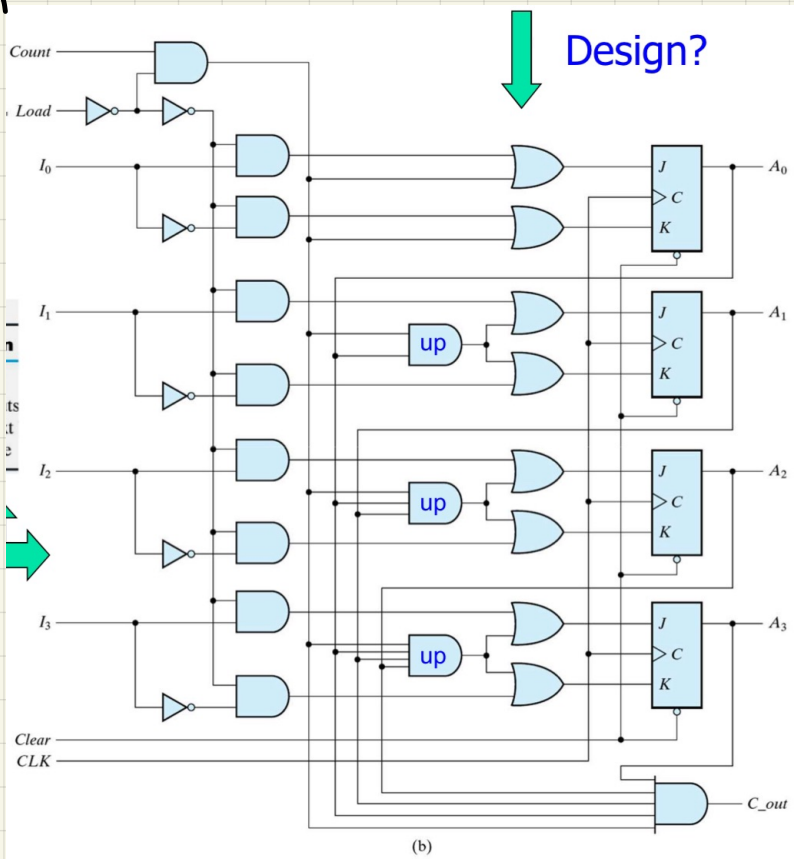




$$\begin{aligned} (a) J_{A0} &= (\text{load } \overline{I_0}) + (\overline{\text{load count}}) \\ K_{A0} &= (\text{load } \overline{I_0}) + (\overline{\text{load count}}) \end{aligned}$$

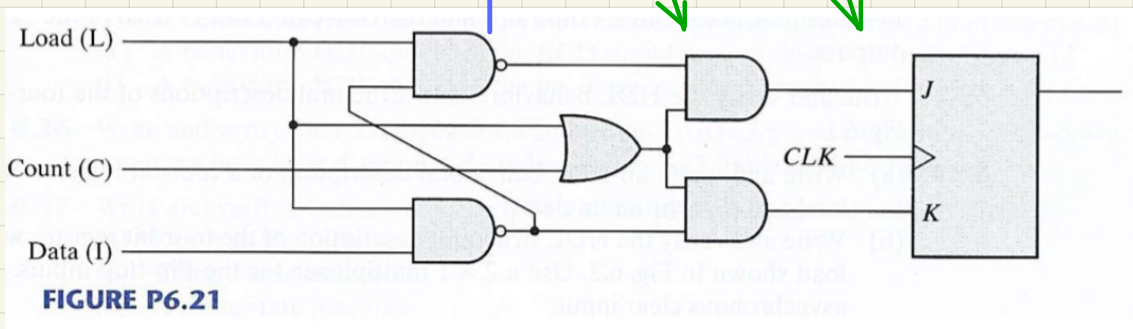[illegible]

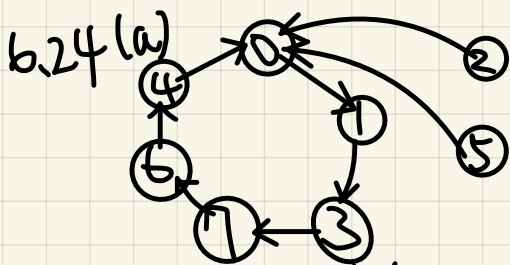


present state next state

Q_4	Q_2	Q_1	Q_4	Q_2	Q_1	T_4	T_2	T_1
0	0	0	0	0	1	0	0	1
0	0	1	0	0	1	0	0	0
0	1	0	0	1	0	0	1	0
0	1	1	0	1	0	0	1	0
1	0	0	1	0	0	0	0	0
1	0	1	1	0	1	0	0	0
1	1	0	1	1	0	0	1	0
1	1	1	1	1	1	0	1	0

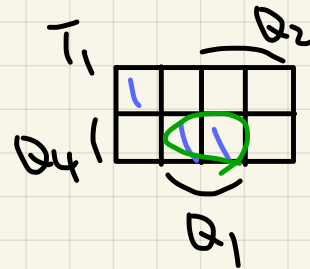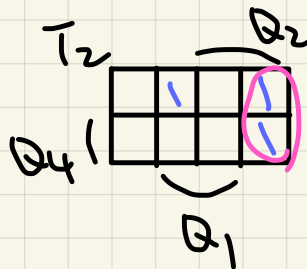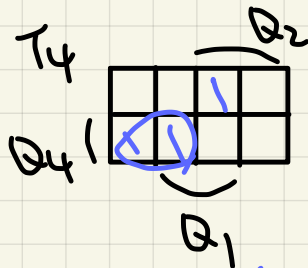

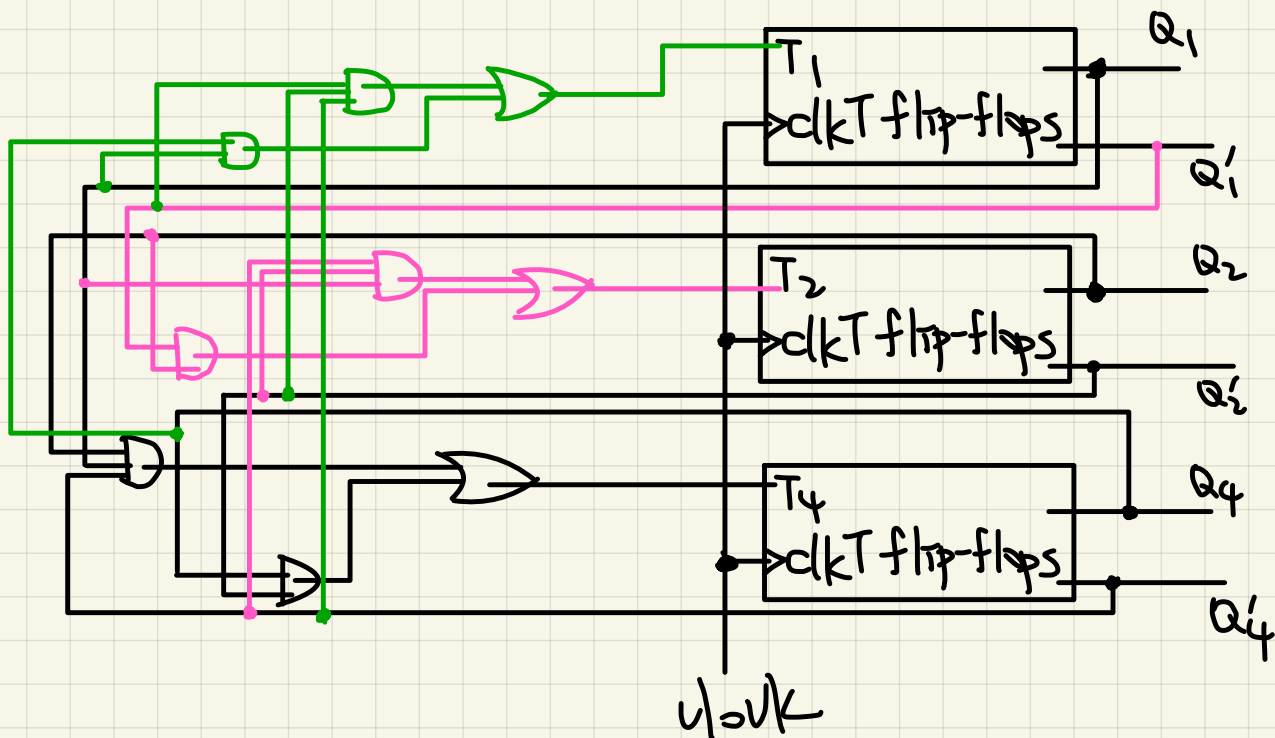
$$T_4 = Q_4 Q_2' + Q_4' Q_2 Q_1 \quad T_2 = Q_2 Q_1' + Q_4' Q_2 Q_1 \quad T_1 = Q_4 Q_1' + Q_4' Q_2 Q_1'$$



(b)


present state next state

Q_4	Q_2	Q_1	Q_4	Q_2	Q_1	T_4	T_2	T_1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	X	X	X	X	X	X
0	1	1	0	0	0	0	0	0
1	0	0	X	X	X	X	X	X
1	0	1	0	0	0	0	0	0
1	1	0	0	1	1	0	1	0
1	1	1	0	1	1	0	1	0

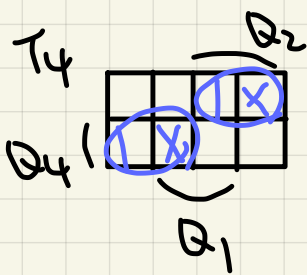


$$T_4 = Q_4 Q_1' + Q_4 Q_1$$

$$= Q_4 \oplus Q_1$$

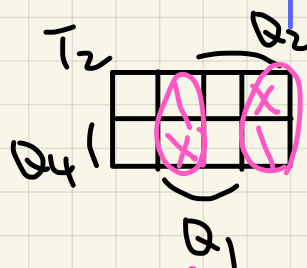

$$T_2 = Q_2 Q_1' + Q_2 Q_1$$

$$= Q_2 \oplus Q_1$$


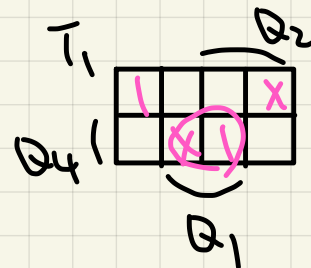


$$T_1 = Q_4 Q_1' + Q_4 Q_1$$


$$= Q_4 \oplus Q_1$$

present state next state

Q_4	Q_2	Q_1	Q_4	Q_2	Q_1	T_4	T_2	T_1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	1	0	0	X	X	X
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	X	X	X
1	0	1	0	1	1	0	1	0
1	1	0	0	1	1	0	1	0
1	1	1	0	1	1	0	1	0


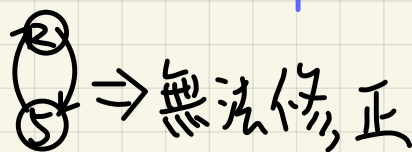
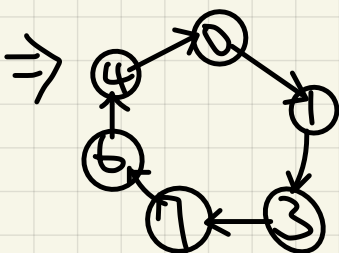


6.28

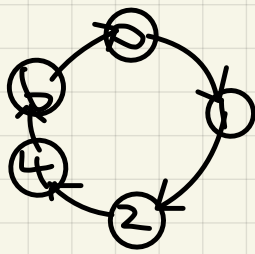

present state next state

Q_4	Q_2	Q_1	Q_4	Q_2	Q_1	D_4	D_2	D_1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
0	1	1	1	1	1	1	1	1
1	0	0	0	0	1	0	0	1
1	0	1	0	1	0	0	1	0
1	1	0	1	0	0	1	0	0
1	1	1	1	1	1	1	1	1

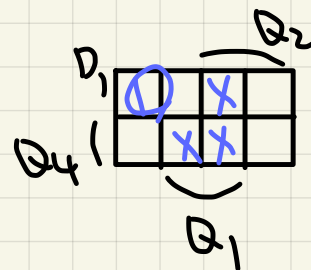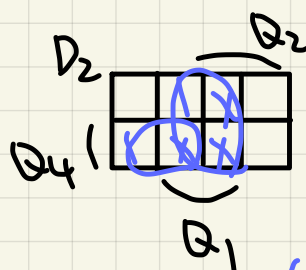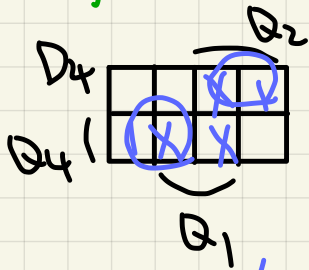

$$D_4 = Q_4 Q_2 + Q_4' Q_2' = Q_4 \oplus Q_2$$

$$D_2 = Q_4 Q_2 + Q_1$$

$$D_1 = Q_4' Q_2' Q_1'$$

