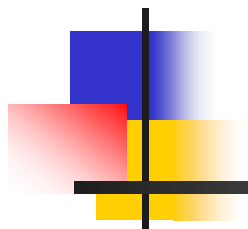



數位電路設計

Digital Circuit Design



莊仁輝

交通大學資訊工程系

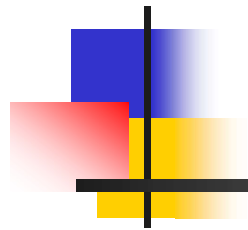

Chapter 2

Boolean Algebra and Logic Gates



2.3 Axiomatic Definitions of Boolean Algebra

- An algebraic structure defined by a set of elements B and **two** binary operators $+$ and \cdot , providing the following **postulates** are satisfied (Boolean Algebra, E. V. Huntington, 1904):
 1. **Closure** w.r.t. the operator $+$ (\cdot)
 2. An **identity** element w.r.t. $+$ (\cdot)
 3. **Commutative** w.r.t. $+$ (\cdot)
 4. \cdot is **distributive** over $+$
 $+$ is **distributive** over \cdot
 5. $\forall x \in B, \exists x' \in B$ (**complement** of x)
 6. \exists at least two elements $x, y \in B$ such that **$x \neq y$**



2.3 Axiomatic Definitions of Boolean Algebra

- Two-valued Boolean Algebra
 - $B = \{0,1\} \rightarrow$ Postulate 6
 - The rules of operations

AND

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT


x	x'
0	1
1	0

Postulate 1

2.4 Basic Theorems and Properties



Table 2.1

Postulates and Theorems of Boolean Algebra



x	y	$x \cdot y$	x	y	$x + y$	x	x'
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Postulate 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

- Duality between (a) and (b): AND  OR, 1  0



2.4 Basic Theorems and Properties

■ Theorem 1(a): $x+x = x$

■ $x+x = (x+x) \text{ 1}$	by postulate:	2(b)
$= (x+x) \text{ (} x+x' \text{)}$		5(a)
$= x+xx'$		4(b)
$= x+0$		5(b)
$= x$		2(a)

■ Theorem 1(b): $xx = x$

■ $xx = x x + 0$
$= xx + xx'$
$= x (x + x')$
$= x 1$
$= x$



2.4 Basic Theorems and Properties

- Theorem 2

- $x + 1 = 1 (x + 1)$
 $= (x + x')(x + 1)$
 $= x + x' 1$
 $= x + x'$
 $= 1$

- $x 0 = 0$ by duality

- Theorem 3: $(x')' = x$

- Postulate 5 defines the complement of x , $x + x' = 1$ and $x x' = 0$
 - The complement of x' is x and is also $(x')'$ (the complement is unique)



2.4 Basic Theorems and Properties

- Theorem 6

- $x + xy = x \cdot 1 + xy$
 $= x(1 + y)$
 $= x \cdot 1$
 $= x$

- $x(x + y) = x$ by duality

- By means of truth table

x	y	xy	$x + xy$
0	0	0	
0	1	0	
1	0	0	
1	1	1	



2.4 Basic Theorems and Properties

- DeMorgan's Theorems

- $(x+y)' = x' y'$
- $(x y)' = x' + y'$

x	y	$x+y$	$(x+y)'$	x'	y'	$x'y'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

- The distributive laws ...



2.4 Basic Theorems and Properties

- Operator Precedence

- parentheses
- NOT
- AND
- OR

- Examples

- $x y' + z$
- $(x y + z)'$



2.5 Boolean Functions

- A Boolean function
 - binary variables
 - binary operators OR and AND
 - unary operator NOT
 - Parentheses

- Examples
 - $F_1 = x + y'z$
 - $F_2 = x' y' z + x' y z + x y'$
 - $F_3 = x y' + x' z$



2.5 Boolean Functions


- $F_1 = x + y'z$
- $F_2 = x' y' z + x' y z + x y'$ 
- $F_3 = x y' + x' z$


Table 2.2
Truth Tables for F_1 and F_2

x	y	z	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

- Two Boolean expressions may specify the same function: $F_2 = F_3$

2.5 Boolean Functions

- Implementation with logic gates

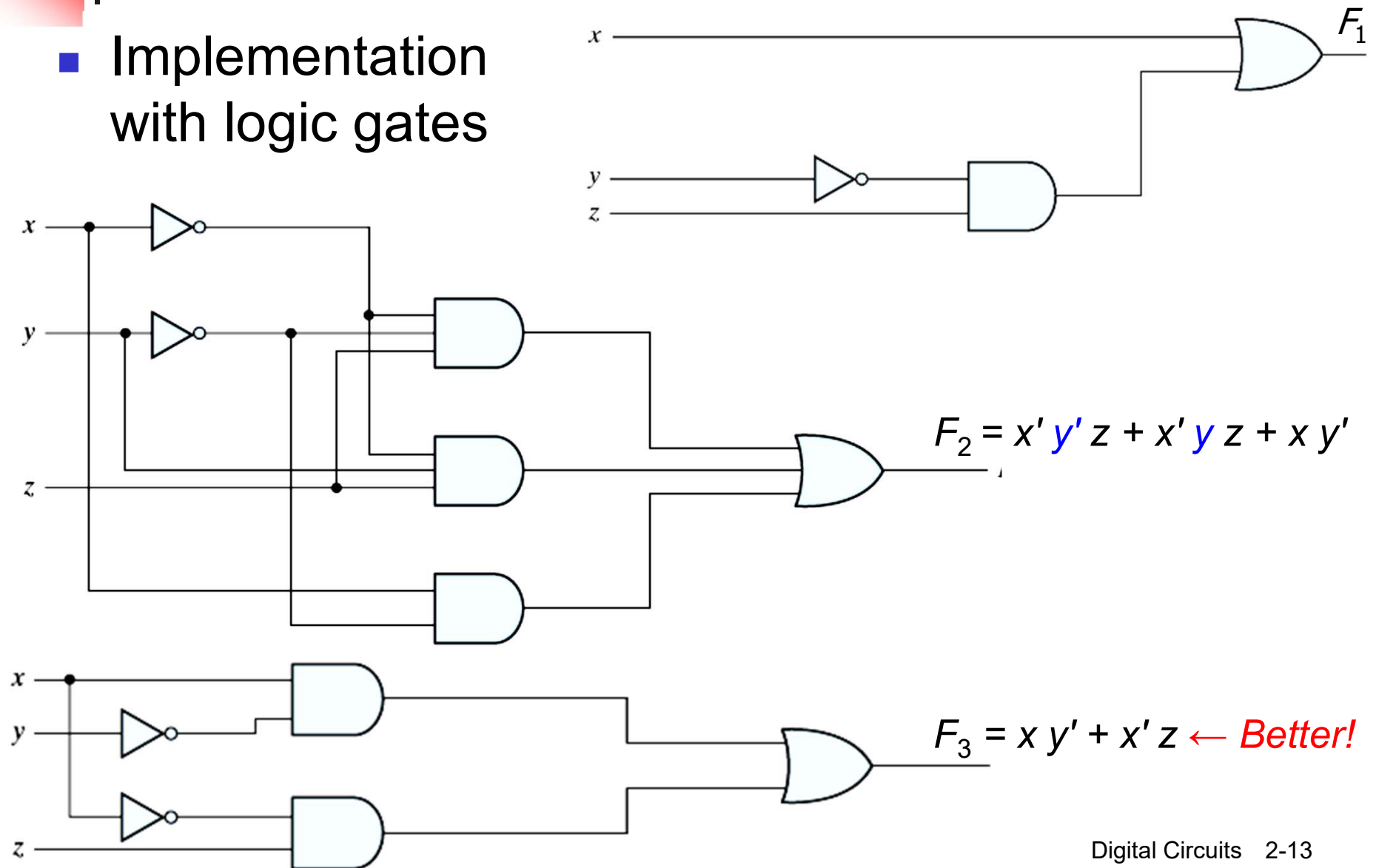



Algebraic Manipulation

- To minimize Boolean expressions
 - **literal**: a primed or unprimed variable (an **input** to a gate)
 - **term**: an implementation with a **gate**
 - The **minimization** of the number of literals and the number of terms → **a circuit with less equipment**
 - It is a hard problem (no specific rules to follow)



Algebraic Manipulation

■ Ex. 2.1

1. $x(x'+y) = xx' + xy = \dots = xy$

2. $x + x'y =$

3. $(x+y)(x+y') =$

4.
$$\begin{aligned} xy + x'z + yz &= xy + x'z + yz(x+x') \\ &= xy + x'z + yzx + yzx' \\ &= xy(1+z) + x'z(1+y) \\ &= xy + x'z \end{aligned}$$

5. $(x+y)(x'+z)(y+z) =$

■ **Duality:** $1 \leftrightarrow 2, 4 \leftrightarrow 5$ (consensus theorem)



Complement of a Function: A or B

A. $F' \leftarrow$ an **interchange** of 0's for 1's and 1's for 0's in the value of F (Table)

B. $F' \leftarrow$ Applying DeMorgan's theorem to F

$$(A+B)' = A'B', (AB)' = A' + B' \text{ (Algebra)}$$

➤ 3-variable DeMorgan's theorem

$$\blacksquare (A+B+C)' = (A+X)'$$

$$\text{let } B+C = X$$

$$= A'X'$$

by DeMorgan's

$$= A'(B+C)'$$

$$= A'(B'C')$$

by DeMorgan's

$$= A'B'C'$$

associative



Complement of a Function

- Generalizations of DeMorgan's theorem

- $(A+B+C+ \dots +F)' = A'B'C' \dots F'$

- $(ABC \dots F)' = A'+B'+C'+ \dots +F'$

- **Ex. 2.2** (use DeMorgan's theorem)

- $(x'yz' + x'y'z)' = (x'yz')' (x'y'z)'$
 $= (x+y'+z) (x+y+z')$

- $[x(y'z'+yz)]' = x' + (y'z'+yz)'$
 $= x' + (y'z')' (yz)'$
 $= x' + (y+z) (y'+z') = \dots$

- **Ex. 2.3** (take the **dual** + **complement** each literal)

- $x'yz' + x'y'z \rightarrow (x'+y+z') (x'+y'+z)$ (the dual)
 $\rightarrow (x+y'+z)(x+y+z')$

- $[x(y'z'+yz)]' \rightarrow \dots$



2.6 Canonical and Standard Forms

■ Minterms and Maxterms

- A minterm: an **AND** term consists of **all literals** (in their normal form or in their complement form)
- For example, **two** binary variables x and y ,
 - $xy, xy', x'y, x'y'$
- It is also called **a standard product**
- **n variables** can be combined to form **2^n minterms**

- A **maxterm**: an **OR** term
- It is also call **a standard sum**
- **2^n maxterms**

2.6 Canonical and Standard Forms

- each **maxterm** is the **complement** of its corresponding **minterm**, and vice versa

Table 2.3

Minterms and Maxterms for Three Binary Variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7



2.6 Canonical and Standard Forms

- A Boolean function can be expressed by
 - a **truth table** or **sum of minterms**
- **Ex.**
 - $f_1 = x'y'z + xy'z' + xyz = m_1 + m_4 + m_7$
 - $f_2 = x'yz + xy'z + xyz' + xyz = m_3 + m_5 + m_6 + m_7$

Table 2.4

Functions of Three Variables

x	y	z	Function f_1	Function f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



2.6 Canonical and Standard Forms

- The **complement** of a Boolean function
 - the minterms that produce a 0
 - $f_1' = m_0 + m_2 + m_3 + m_5 + m_6$
 $= x'y'z' + x'yz' + x'yz + xy'z + xyz'$
 - $f_1 = (f_1')'$
 $= (x+y+z)(x+y'+z)(x+y'+z')(x'+y+z')(x'+y'+z)$
 $= M_0 M_2 M_3 M_5 M_6$
 - Any Boolean function can be expressed as
 - a sum of minterms
 - a product of maxterms→ **canonical** forms



2.6 Canonical and Standard Forms

■ Ex. 2.4 Sum of minterms

■ $F = A + B'C$

$$= A(B + B') + B'C$$

$$= AB + AB' + B'C$$

$$= AB(C + C') + AB'(C + C') + (A + A')B'C$$

$$= ABC + ABC' + AB'C + AB'C' + A'B'C$$

$$= m_1 + m_4 + m_5 + m_6 + m_7$$

■ $F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$

■ or, built the truth table first →

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



2.6 Canonical and Standard Forms

■ Ex. 2.5 Product of maxterms

- $F = xy + x'z$
$$= (xy + x')(xy + z)$$
$$= (x+x')(y+x')(x+z)(y+z)$$
$$= (x'+y)(x+z)(y+z)$$
- $x'+y = x' + y + zz'$
$$= (x'+y+z)(x'+y+z')$$
- $F = (x+y+z)(x+y'+z)(x'+y+z)(x'+y+z')$
$$= M_0 M_2 M_4 M_5$$
- $F(x,y,z) = \Pi(0,2,4,5)$



Conversion between Canonical Forms

- Example

$$F(A,B,C) = \Sigma(1,4,5,6,7)$$

$$F'(A,B,C) = \Sigma(0,2,3)$$

$$F(A,B,C) = \Pi(0,2,3)$$

(By DeMorgan's theorem: $m_j' = M_j$)

- sum of minterms \leftrightarrow product of maxterms
 - interchange the symbols Σ and Π and list those numbers missing from the original form
 - Σ of 1's
 - Π of 0's



Conversion between Canonical Forms

■ Example

- $F(x, y, z) = \Sigma(1, 3, 6, 7)$
- $F(x, y, z) = \Pi(0, 2, 4, 5)$

Table 2.6

Truth Table for $F = xy + x'z$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Consensus theorem: $xy + x'z + yz = xy + x'z$
 - **redundant term** → can eliminate **race hazards**



Standard Forms

- **Canonical** forms are seldom used
- Sum of products (**SOP**)

$$F_1 = y' + zy + x'yz'$$

- Product of sums (**POS**)


$$F_2 = x(y'+z)(x'+y+z'+w)$$

- **Nonstandard** form \rightarrow standard form


$$\begin{aligned} F_3 &= AB + C(D+E) \\ &= AB + CD + CE \end{aligned}$$

Standard Forms

■ Two-level implementation

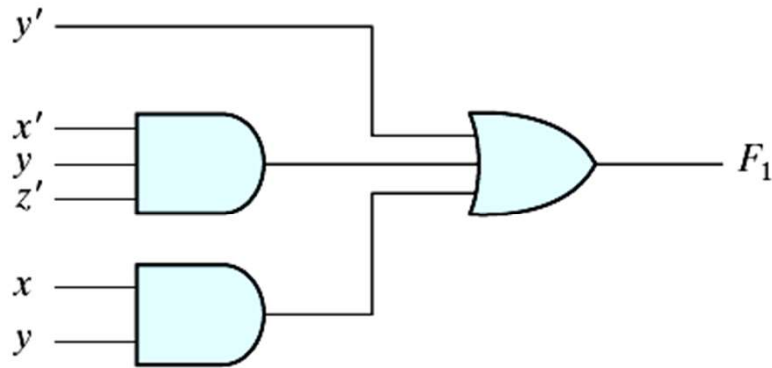


(a) Sum of Products

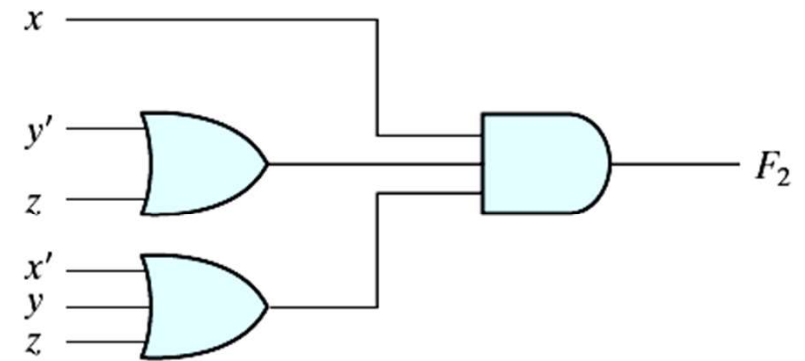


(b) Product of Sums

■ Three- and two-level implementation

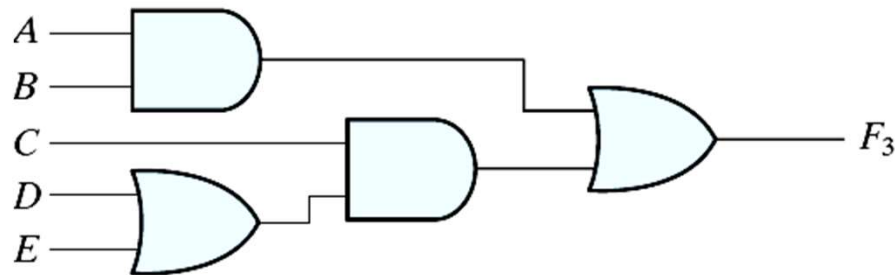

(a) $AB + C(D + E)$

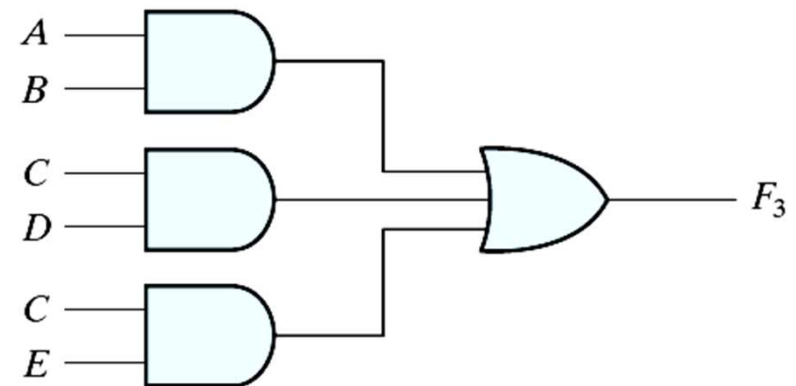

(b) $AB + CD + CE$



2.7 Other Logic Operations

- 2^n rows in the truth table of n binary variables
- 2^{2^n} functions for n binary variables
- 16 functions of two binary variables

Table 2.7

Truth Tables for the 16 Functions of Two Binary Variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

- All the new symbols except for the **exclusive-OR** symbol are not in common use by digital designers

Table 2.8**Boolean Expressions for the 16 Functions of Two Variables**

Boolean Functions	Operator Symbol	Name	Comments
0000 $F_0 = 0$		Null	Binary constant 0
0001 $F_1 = xy$	$x \cdot y$	AND	x and y
0010 $F_2 = xy'$	x/y	Inhibition	x , but not y
0011 $F_3 = x$		Transfer	x
0100 $F_4 = x'y$	y/x	Inhibition	y , but not x
0101 $F_5 = y$		Transfer	y
0110 $F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y , but not both
0111 $F_7 = x + y$	$x + y$	OR	x or y
1000 $F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
1001 $F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
1010 $F_{10} = y'$	y'	Complement	Not y
1011 $F_{11} = x + y'$	$x \subset y$	Implication	If y , then x
1100 $F_{12} = x'$	x'	Complement	Not x
1101 $F_{13} = x' + y$	$x \supset y$	Implication	If x , then y
1110 $F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
1111 $F_{15} = 1$		Identity	Binary constant 1



2.8 Digital Logic Gates





- Boolean **expressions**: AND, OR and NOT operations
- Constructing gates of other logic operations
 - the **feasibility** and **economy**
 - the possibility of **extending** gate's **inputs**
 - the **basic properties** of the binary operations
 - the ability of the gate to implement Boolean functions **alone** or ...



2.8 Digital Logic Gates


- Consider the 16 functions
 - two are equal to a constant
 - four are repeated
 - inhibition and implication are not commutative or associative
 - the other **eight**: complement, transfer, AND, OR, NAND, NOR, XOR, and equivalence are used as **standard gates**

Standard Gates

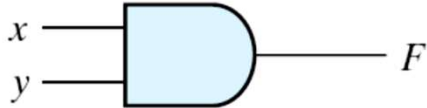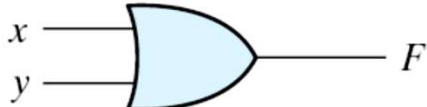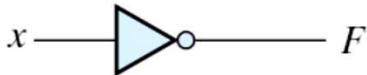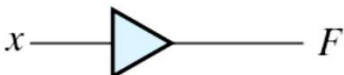Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = xy$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	


Standard Gates

NAND

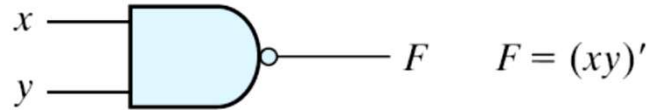


x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

NOR

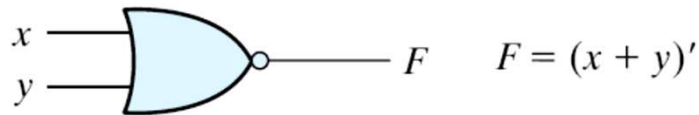


x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive-OR
(XOR)

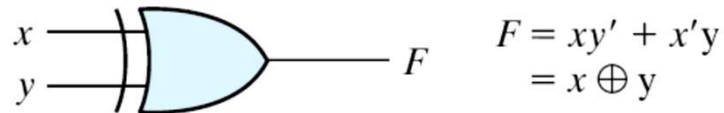

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0


Exclusive-NOR
or
equivalence
(XNOR)

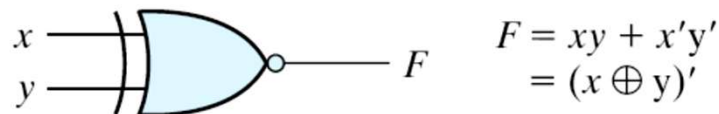

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

Extension to Multiple Inputs

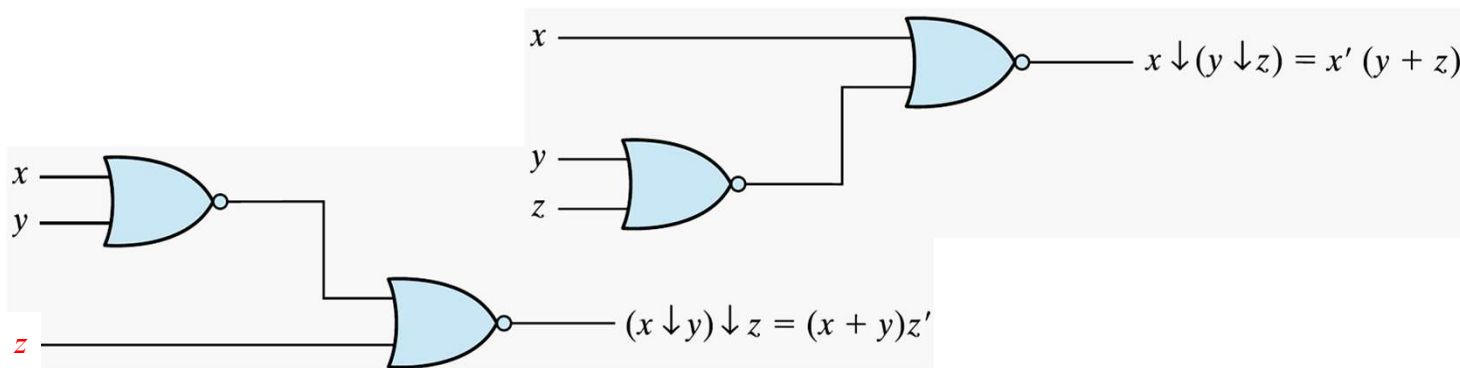
- **AND** and **OR** are commutative and associative
 - $(x+y)+z = x+(y+z) = x+y+z$
 - $(x \cdot y)z = x(y \cdot z) = x \cdot y \cdot z$
- **NAND** and **NOR** are commutative but **not associative** → they are **not extendable**




→ $(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$

Extension to Multiple Inputs

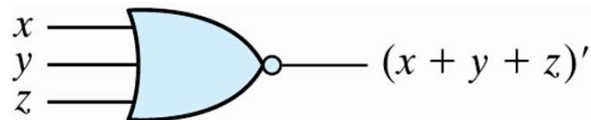- Multiple NOR \triangleq a **complemented OR** gate
- Multiple NAND \triangleq a **complemented AND** gate




(a) 3-input NOR gate

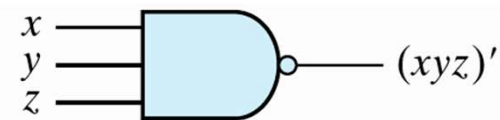


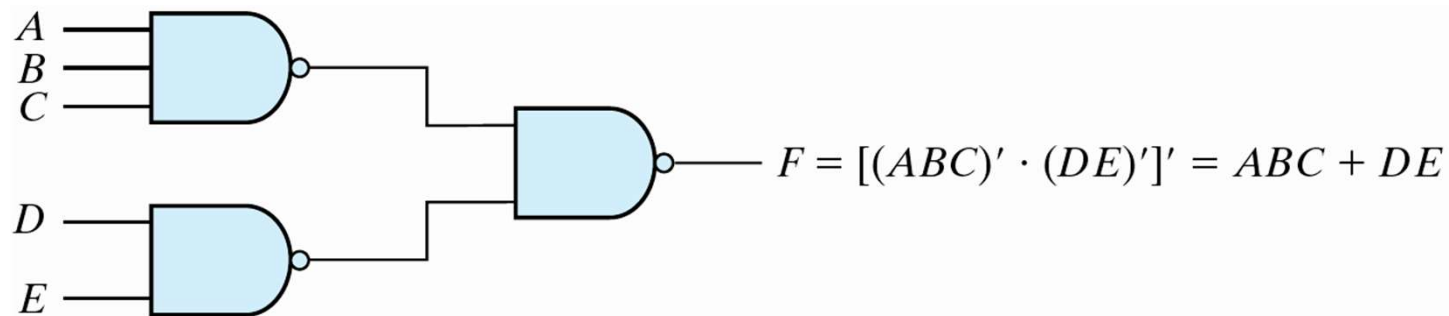(b) 3-input NAND gate

- The **cascaded NAND** operations = **sum of products**
- The **cascaded NOR** operations = **product of sums**





(c) Cascaded NAND gates

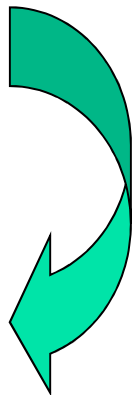

Extension to Multiple Inputs

- The **XOR** and **XNOR** gates are **commutative** and **associative**

- Example: 3-input XOR gate

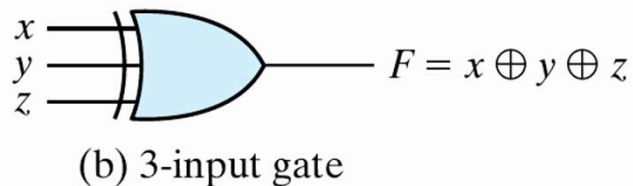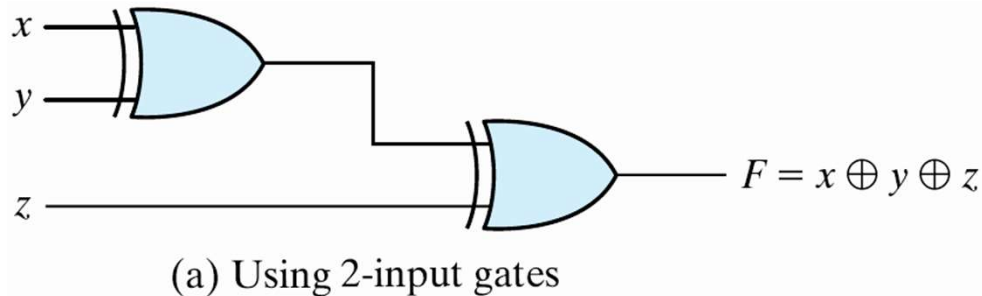

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table

- XOR is an **odd function**: it is equal to 1 if the inputs variables have an odd number of 1's

Positive and Negative Logic

x	y	z
L	L	L
L	H	L
H	L	L
H	H	H


(a) Truth table with H and L

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1


(c) Truth table for positive logic

x	y	z
1	1	1
1	0	1
0	1	1
0	0	0


(e) Truth table for negative logic

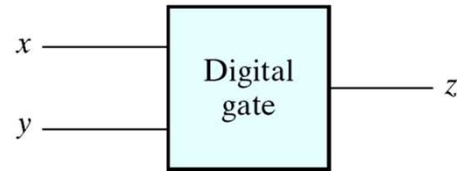

(b) Gate block diagram

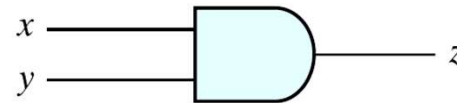



(d) Positive logic AND gate

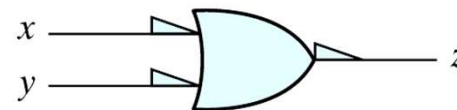

(f) Negative logic OR gate

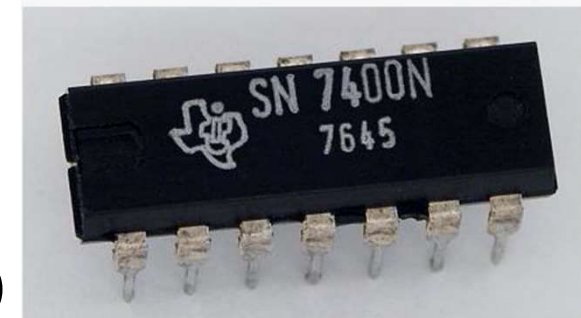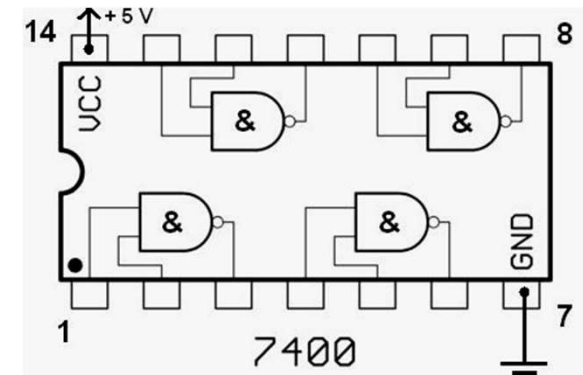2.9 Integrated Circuits (IC, chips)

- Levels of integration
 - **SSI**: < 10 gates
 - **MSI**: 10 ~ 1000 gates (Chapter 4)
 - **LSI**: 1000 ~ 100k gates (Chapter 7)
 - **VLSI**: > 100k gates
 - small size (compact size)
 - low cost
 - low power consumption
 - high reliability
 - high speed



(from wikipedia)




2.9 Integrated Circuits

- Digital logic families: circuit technology
 - **TTL**: transistor-transistor logic
 - **ECL**: emitter-coupled logic (high speed, high power consumption)
 - **MOS**: metal-oxide semiconductor (NMOS, high density)
 - **CMOS**: complementary MOS (low power)
 - **BiCMOS**: high speed, high density

2.9 Integrated Circuits

■ CMOS circuit

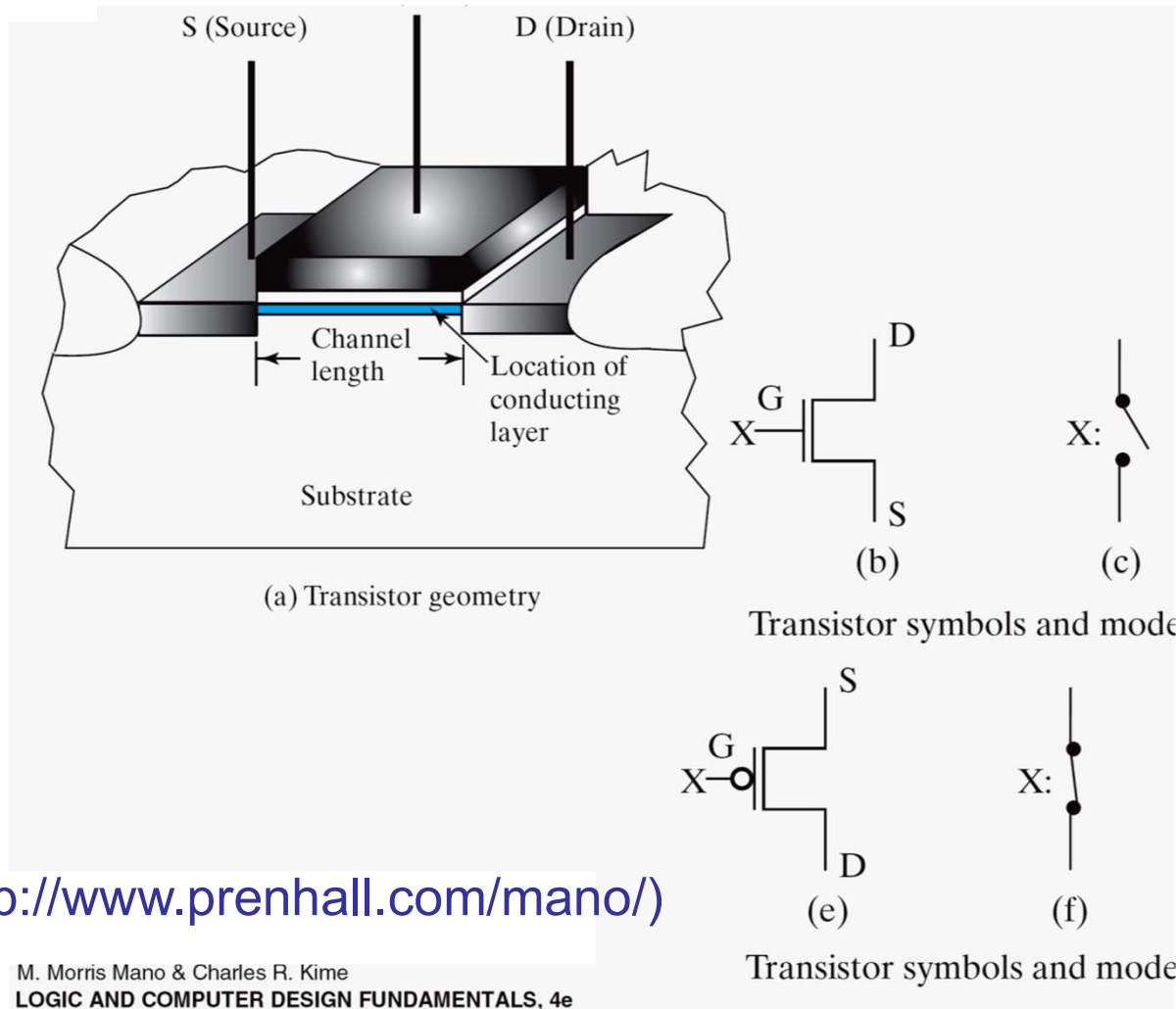


(from: <http://www.prenhall.com/mano/>)


M. Morris Mano & Charles R. Kime
LOGIC AND COMPUTER DESIGN FUNDAMENTALS, 4e

2.9 Integrated Circuits


Logic 1 $\leftarrow x = y = 0$

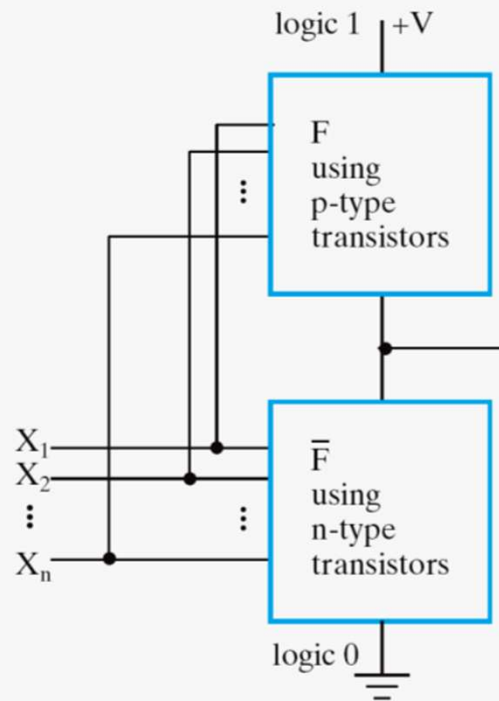


(a) General structure

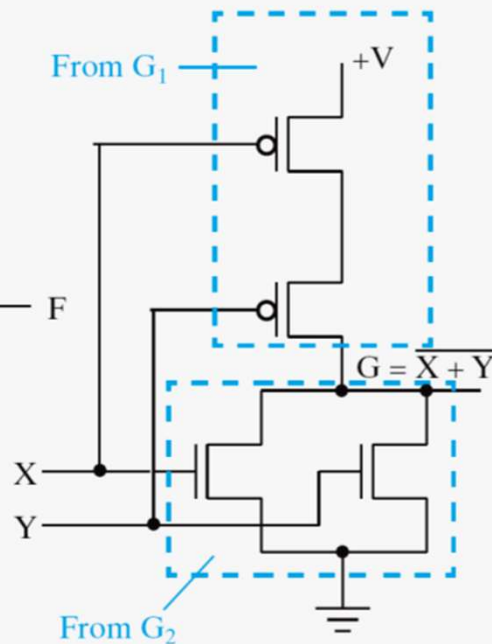

(b) NOR

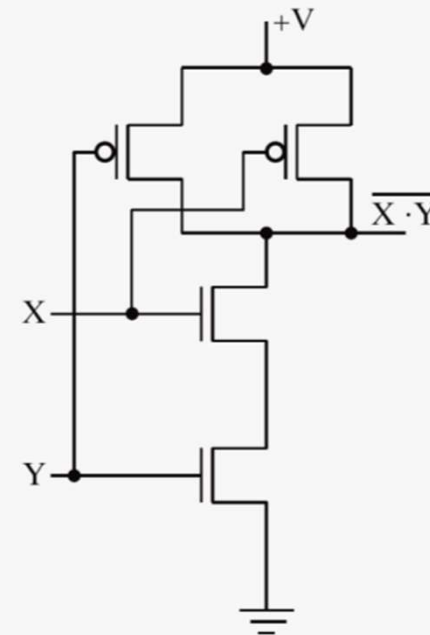

(c) NAND

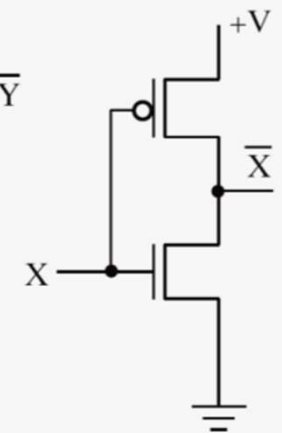


(d) NOT

Logic 0 $\leftarrow x = 1$ or $y = 1$

(better than NOR)

2.9 Integrated Circuits

- NMOS circuit

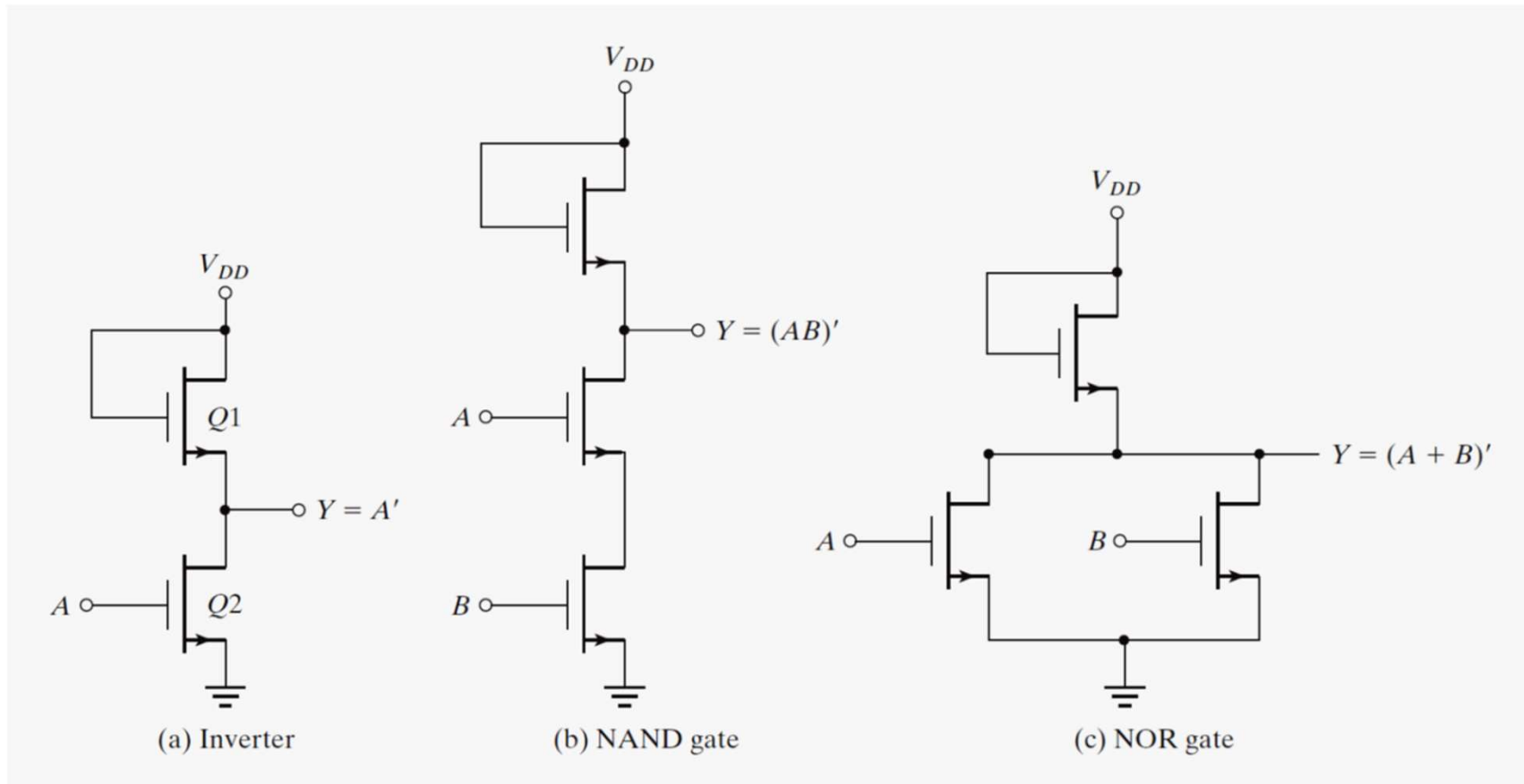



2.9 Integrated Circuits

- The most important parameters
 - **Fan-out**: the number of standard loads that the output of a typical gate can drive
 - **Fan-in**: ...
 - **Power dissipation**
 - **Propagation delay**: the average transition delay time for the signal to propagate from input to output
 - **Noise margin**: the maximum external noise voltage added to an input signal ...



2.9 Integrated Circuits

- Computer-Aided Design (CAD) tools
 - Millions of transistors → software programs
 - Support computer-based representation
 - Automate the design process
- A typical design flow
 - Design entry
 - Schematic capture
 - HDL – Hardware Description Languages (Verilog, VHDL)
 - Simulation
 - Physical realization (ASIC, FPGA, PLD)

2.9 Integrated Circuits

- Ex. A digital version of oscilloscope
 - an analog one:

