

(a) 
$$T_1 = B'C$$
,  $T_2 = A'B$ ,  $T_3 = A + T_1 = A + B'C$ ,  
 $T_4 = D \oplus T_2 = D \oplus (A'B) = A'BD' + D(A + B') = A'BD' + AD + B'D$   
 $F_1 = T_3 + T_4 = A + B'C + A'BD' + AD + B'D$   
With  $A + AD = A$  and  $A + A'BD' = A + BD'$ :  
 $F_1 = A + B'C + BD' + B'D$   
Alternative cover:  $F_1 = A + CD' + BD' + B'D$ 


$$F_2 = T_2 + D' = A'B + D'$$

ABCD	$T_1$	$T_2$	$T_3$	$T_4$	$F_1$	$F_2$
0000	0	0	0	0	0	1
0001	0	0	0	1	1	0
0010	1	0	1	0	1	1
0011	1	0	1	1	1	0
0100	0	1	0	1	1	1
0101	0	1	0	0	0	1
0110	0	1	0	1	1	1
0111	0	1	0	0	0	1
1000	0	0	1	0	1	1
1001	0	0	1	1	1	0
1010	1	0	1	0	1	1
1011	1	0	1	1	1	0
1100	0	0	1	0	1	1
1101	0	0	1	1	1	0
1110	0	0	1	0	1	1
1111	0	0	1	1	1	0
	1					

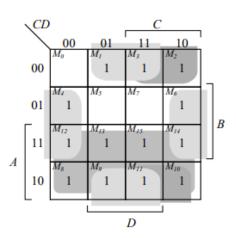


$$F_1 = A + B'C + B'D + BD'$$

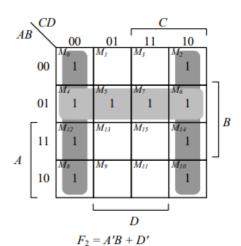

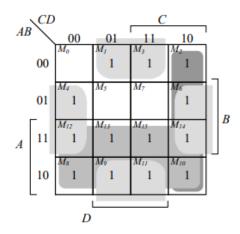

$$F_1 = A + CD' + B'D + BD'$$
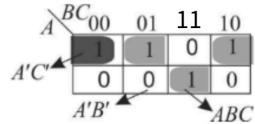
## **4.4** (a) $F(A, B, C) = \Sigma(0, 1, 2, 7)$



## Simplified SOP form:


$$F(A, B, C) = A'C' + A'B' + ABC$$

$$= A'(B' + C') + ABC$$

$$= A'(BC)' + ABC$$

$$= A XNOR (BC)$$

$$=A \oplus (BC)$$

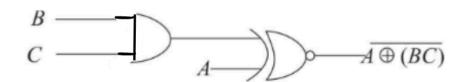


Decimal	8, 4, -2, -1  code				BCD Code			
Digit	$\overline{w}$	x	y	z	A	B	C	D
0	0	0	0	0	0	0	0	0
1	0	1	1	1	0	0	0	1
2	0	1	1	0	0	0	1	0
3	0	1	0	1	0	0	1	1
4	0	1	0	0	0	1	0	0
5	1	0	1	1	0	1	0	1
6	1	0	1	0	0	1	1	0
7	1	0	0	1	0	1	1	1
8	1	0	0	0	1	0	0	0
9	1	1	1	1	1	0	0	1


$$A = wx + wy'z'$$

$$B = x'z + x'y + xy'z'$$

$$C = y \oplus z$$

$$D = z$$

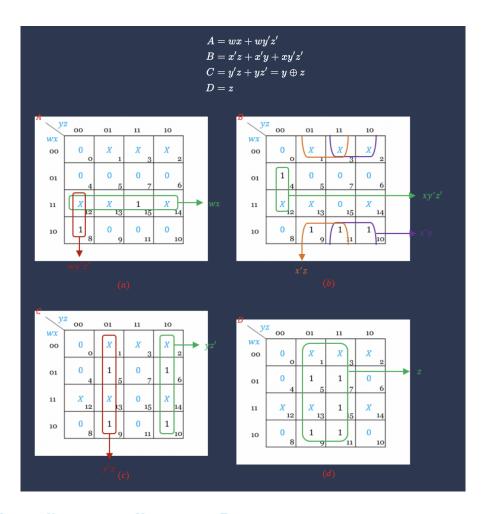

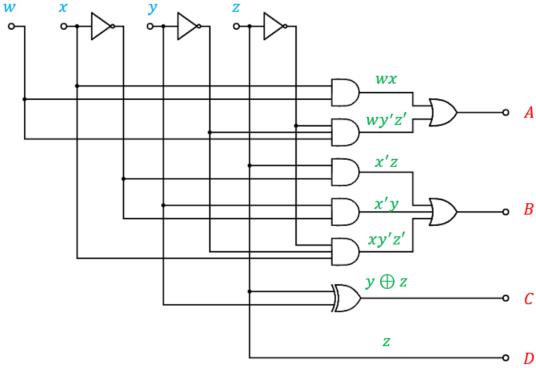

**4.14** xor AND OR XOR 10 + 5 + 5 + 10 = 30 ns

